

UNIVERSITI MALAYSIA PERLIS

Peperiksaan Akhir Semester Kedua  
Sidang Akademik 2018/2019

Mac 2019

**DKT 123 – Teknologi Elektrik**  
**[Electrical Technology]**

Masa: 3 Jam

---

Please make sure that this paper has **ELEVEN (11)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **SEBELAS (11)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This question paper contains **TWO (2)** parts:

*[Kertas soalan ini mengandungi **DUA (2)** bahagian:]*

**Part A** : This part has **FOUR (4)** questions. Answer all questions (80 marks).  
*[Bahagian A : Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab semua soalan (80 markah).]*

**Part B** : This part has **TWO (2)** questions. Answer any **ONE (1)** question (20 marks).  
*[Bahagian B : Bahagian ini mengandungi **DUA (2)** soalan. Jawab mana-mana **SATU (1)** soalan (20 markah).]*

Each question contributes **TWENTY (20)** marks.

*[Setiap soalan menyumbang **DUA PULUH (20)** markah.]*

## PART A

*[BAHAGIAN A]*

Answer all questions

*[Jawab semua soalan]*

## Question 1

*[Soalan 1]*

- (a) State TWO(2) advantages of three phase system and explain the condition where the three phase system is said to be in balanced.

*[Senaraikan DUA(2) kelebihan sistem tiga fasa dan jelaskan keadaan di mana sistem tiga fasa dikatakan berada dalam keseimbangan.]*



(4 Marks/Markah)

- (b) A wye-connected balanced three-phase voltage sources is connected to a wye-connected balanced load with an impedance of  $(3+j7) \Omega$  per phase. If  $V_{an} = 100 \angle 45^\circ V$  and the voltages are in positive sequence,

*[Satu sumber seimbang voltan tiga-fasa yang disambung secara wye bersambung dengan beban seimbang sambungan delta dengan galangan  $(3 + j7) \Omega$  per fasa. Jika  $V_{an} = 100 \angle 45^\circ V$  dan voltan dalam juyukan positif.]*

- i. Draw the diagram of this three-phase system configuration and label its parameter accordingly.

*[Lukiskan gambarajah tatarajah sistem tiga-fasa ini dan labelkan parameter dengan seujarnya.]*

(4 Marks/Markah)

- ii. Calculate the average power per phase  $P_p$  and total average power  $P_T$ .

*[Kira purata kuasa per fasa  $P_p$  dan jumlah purata kuasa  $P_T$ .]*

$$P_p = \sqrt{3} V I \cos \phi$$

(3 Marks/Markah)

$$P_p = 384$$

- iii. Calculate the reactive power per phase  $Q_p$  and total reactive power  $Q_T$ .

*[Kira kuasa regangan per fasa  $Q_p$  dan jumlah kuasa regangan  $Q_T$ .]*


$$Q_p = \sqrt{3} V I \sin \phi$$

(3 Marks/Markah)

$$Q_p = 309$$

-3-

- (c) Evaluate the following circuit in **Figure 1** using mesh analysis to find current  $I_o$ .  
[Nilaikan litar dalam **Rajah 1** berikut menggunakan analisis jejaring untuk mencari nilai  $I_o$ .]

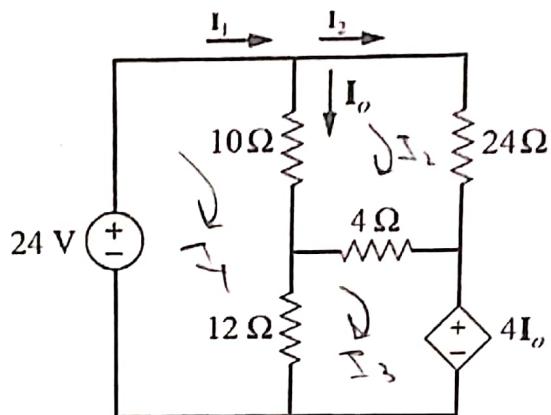

**Figure 1**  
[Rajah 1]

(6 Marks/Markah)

**Question 2***[Soalan 2]*

- (a) Coupling coefficient ( $k$ ) is the measure of magnetic coupling between two coils.  
*[Pekali gandingan ( $k$ ) adalah ukuran gandingan magnet antara dua gegelung.]*

- (i) Define  $k$  when the condition as follow:  
*[Definisikan  $k$  apabila keadaan seperti berikut:]*


$$k > 0.5$$

$$k < 0.5$$

(2 Marks/Markah)

- (ii) Given the circuit as in Figure 2, and  $k = 1$  where  
*[Diberi litar seperti Rajah 2 dan  $k = 1$  di mana]*

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

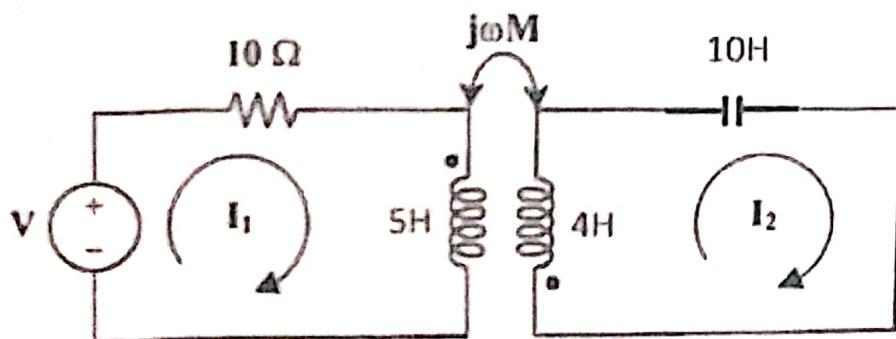

**Figure 2**  
*[Rajah 2]*


Evaluate the value for phasor current  $I_1$  and  $I_2$  given that  
*[Hitungkan nilai untuk arus pemfasa  $I_1$  dan  $I_2$  diberi]*

$$V = 60 \cos(4t + 30^\circ) V$$

(6 Marks/ Markah)

-5-

- (b) Dot determination is required to specify the polarity of mutual induced voltage. With appropriate figure, interpret the application of the dot convention.  
*[Penentuan bintik diperlukan untuk menentukan keikutuan voltan saling teraruh. Dengan gambarajah yang sesuai, tafsirkan penggunaan kelaziman bintik.]*
- (6 Marks/Markah)
- (c) Calculate the mesh currents in the circuit shown in Figure 3.  
*[Hitung arus jejaring dalam litar pada Rajah 3.]*

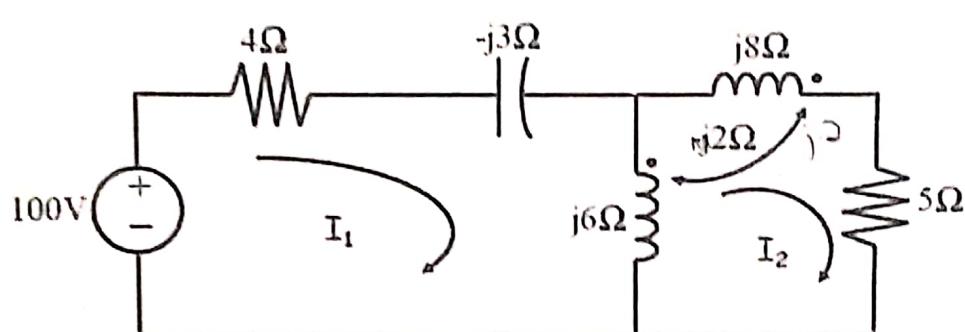

**Figure 3**  
*[Rajah 3]*

(6 Marks/Markah)


Ans 3

-1  
2

-1  
2

**Question 3**  
*[Soalan 3]*

- (a) With the aid of a suitable diagram briefly explain the concept of mutual inductance.  
*[Dengan bantuan gambarajah yang sesuai terangkan secara ringkas konsep aruhan saling.]*  
 (4 Marks/Markah)
- (b) Briefly discuss THREE(3) differences between an electric circuit and magnetic circuit.  
*[Bincangkan secara ringkas TIGA (3) perbezaan di antara litar elektrik dan litar magnet.]*  
 (3 Marks/Markah)
- (c) If one section of the existing core material is replaced with cast iron whose relative permeability is 166 and flux of 1 mWb flows in the circuit as shown in Figure 4, determine the followings:  
 (Given  $\mu_0 = 4\pi \times 10^{-7}$ )  
*[Sekiranya satu bahagian bahan teras sedia ada digantikan dengan besi tuang yang kebolehtelapan relatif 166 dan aliran fluks 1 mWb dalam litar seperti ditunjukkan dalam Rajah 4, tentukan yang berikut:]*  
*(Diberi  $\mu_0 = 4\pi \times 10^{-7}$ )*

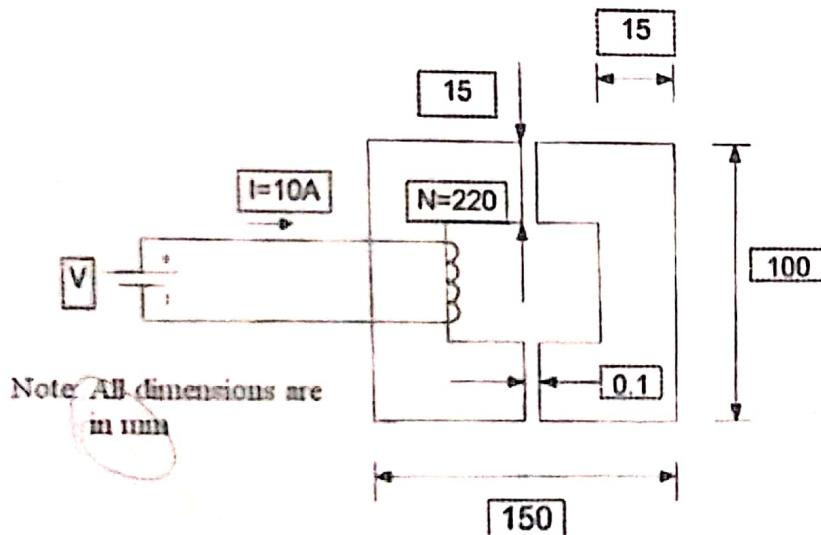

**Figure 4**  
*[Rajah 4]*

- i. the resultants mean length of flux path the each core made by the air gaps.  
*[Panjang paduan min untuk lajuan fluks pada setiap teras yang dihasilkan oleh jurang udara]*  
 (4 Marks/Markah)
- ii. magnetic flux densities in each core and air gap.  
*[Ketumpatan fluks magnet dalam setiap teras dan jurang udara]*  
 (3 Marks/Markah)

- iii. Magnetic field strength in each core and air gap.  
*[Kekuatan medan magnet pada setiap teras dan jurang udara.]*

(3 Marks/Markah)

- iv. The reluctances in each core and air gap.  
*[Engganan pada setiap teras dan jurang udara.]*

(3 Marks/Markah)

**Question 4**  
*[Soalan 4]*

- (a) Explain the meaning of the device Transformer and state **TWO (2)** types of Transformer.

*[Jelaskan maksud peranti Pengubah dan nyatakan DUA(2) jenis Pengubah.]*

(4 Marks/Markah)

- (b) Power transformer has two types of core. Name both types and explain their differences.

*[Pengubah kuasa mempunyai dua jenis teras. Namakan kedua-duanya jenis dan terangkan perbezaannya.]*

(4 marks/Markah)

- (c) Consider an ideal single-phase 2400V-240V transformer. The primary is connected to a 2000V source and the secondary is connected to an impedance of  $2\angle36.9^\circ\Omega$ , calculate,

*[Andaikan sebuah pengubah unggul fasa tunggal 2400V-240V. Yang utama disambungkan ke punca 2000V dan yang kedua disambungkan ke galangan  $2\angle36.9^\circ\Omega$ , hitung.]*

- i. the secondary output current and voltage.  
*[Arus dan voltan keluaran kedua.]*

(3 Marks/Markah)

- ii. the primary input current.  
*[Arus masukan utama.]*

(3 Marks/Markah)

- iii. the load impedance as seen from the primary side.  
*[Galangan beban yang dilihat dari sudut utama.]*

(3 Marks/Markah)

- iv. the input and output apparent power.  
*[Masukan dan keluaran kuasa ketara.]*

(3 Marks/Markah)

$$\begin{aligned} V &= IR \\ I^2R &= V \\ I &= \sqrt{\frac{V}{R}} \\ \text{Power} &= I^2 R \end{aligned}$$

**PART B****[BAHAGIAN B]****Answer any ONE (1) question****[Jawab mana-mana SATU (1) soalan]****Question 5****[Soalan 5]**

- (a) State **FOUR (4)** categories of losses occurring in DC machine.  
*[Nyatakan EMPAT (4) kategori kehilangan yang berlaku pada mesin DC.]*

(4 Marks/ Markah)

- (b) Permanent magnet, separately excited and self-excited are three types of DC machine. Compare the differences between separately excited and self excited DC machine. Draw the equivalent circuit for both DC machine.  
*[Magnet kekal, menguja terpisah dan menguja sendiri adalah tiga jenis mesin DC. Bandingkan perbezaan antara mesin DC penguja terpisah dan menguja sendiri. Lukiskan litar setara bagi kedua-dua mesin DC ini.]*

(6 Marks/Markah)

- (c) A 240V DC shunt motor draws 12A at 2000rpm. The armature resistance is  $0.5\Omega$  and field winding resistance is  $450\Omega$ .  
*[Sebuah motor pirau DC 240V menarik 12A pada 2000rpm. Rintangan angker ialah  $0.5\Omega$  dan rintangan medan penggulungan ialah  $450\Omega$ .]*

- i. Calculate the value of the torque  
*[Kira nilai daya kilas]*

(5 Marks/Markah)

- ii. Calculate the speed and line current at a torque of 20 N-m (if field current is constant)  
*[Kira kelajuan dan arus baris pada 20 N-m daya kilas (jika arus medan adalah malar)]*

(5 Marks/Markah)

**Question 6***[Soalan 6]*

- (a) State the first and second law of Faraday's Law.  
*[Nyatakan hukum pertama dan kedua bagi Hukum Faraday.]* (4 Marks/*Markah*)
- (b) Elaborate the main part in synchronous machines.  
*[Perihalkan bahagian utama dalam mesin segerak.]* (6 Marks/*Markah*)
- (c) A three-phase, wye-connected 2300 kVA and 6.6 kV generator operates at full-load. The per-phase armature resistance  $R_a$  and the synchronous reactance,  $X_d$ , are  $(0.06+j10.5)\Omega$ . Calculate the percent voltage regulation at  
*[Sebuah tiga fasa dengan sambungan wai 2300 kVA dan 6.6 kV penjana beroperasi pada beban penuh. Rintangan angker per fasa  $R_a$  dan regangan segerak  $X_d$  ialah  $(0.06+j10.5)\Omega$ . Kirakan peratus peraturan voltan pada.]*
- (i) 0.8 power-factor lagging  
*[0.8 faktor-kuasa susulan]* (5 Marks/*Markah*)
- (ii) 0.8 power-factor leading.  
*[0.8 faktor-kuasa mendulu]* (5 Marks/*Markah*)

**Appendix 1***[Lampiran 1]*

Given some theorem:

*[Diberi sebahagian teorem:]*

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{ab}/-120^\circ$ $V_{ca} = V_{ab}/+120^\circ$ $I_a = V_{an}/Z_Y$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Y-Δ	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ $I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{BC} = V_{ab}/-120^\circ$ $V_{ca} = V_{CA} = V_{ab}/+120^\circ$ $I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Δ-Δ	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$ $I_{AB} = V_{ab}/Z_\Delta$ $I_{BC} = V_{bc}/Z_\Delta$ $I_{CA} = V_{ca}/Z_\Delta$	Same as phase voltages
Δ-Y	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$ Same as line currents	$I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$ Same as phase voltages
		$I_a = \frac{V_p/-30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$