

DKT217/3

COMPUTER SYSTEM
[SISTEM KOMPUTER]
SOLUTION

CONTINUOUS ASSESSMENT

DATE WEDNESDAY, 15th APRIL 2020
TIME 10.00pm ~ 11.00pm (1 hour)

INSTRUCTIONS

- Use your own paper to answer.
- Answers must be handwritten.
- Your name, matric and page number **MUST** be written on every answer page.
- Scan and save in PDF format only.
- Upload/Email the PDF file **BEFORE** 10.55pm
- For Quartus II projects, make sure all your projects are in a folder with the foldername **YOUR NAME** and **MATRIC** as proof of work.

QUESTION 1

- (a) Figure 1 below is a diagram of a bit register. Using the VHDL code, complete the programme for the bit register as in Figure 2.

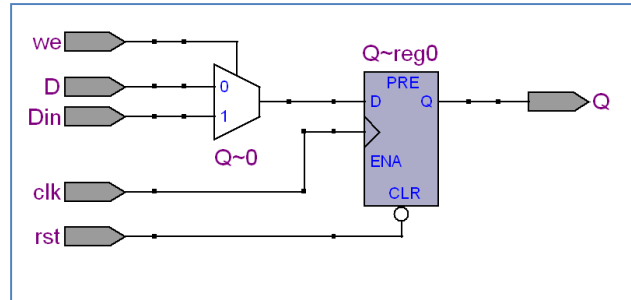


Figure 1: Schematic of a bit register

```
LIBRARY IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY bit_reg IS
PORT ( we, D, Din, clk, rst : IN  STD_LOGIC;
      Q : OUT STD_LOGIC );
END bit_reg;

ARCHITECTURE beh OF bit_reg IS
BEGIN
    PROCESS ( we, D, Din, clk, rst )
    BEGIN
        IF rst = '0' THEN
            Q <= '0';
        ELSIF clk'event and clk = '1' THEN
            IF we = '1' THEN
                Q <= Din;
            ELSE
                Q <= D;
            END IF
        END IF;
    END PROCESS;
END beh;
```

Figure 2: VHDL programme of a bit register

- (b) Figure 3 below is a schematic diagram of the bit register in Question 1(a) connected together to become a 4 bit shift-right register. An incomplete VHDL program is shown below. Complete the program to satisfy Figure 3.

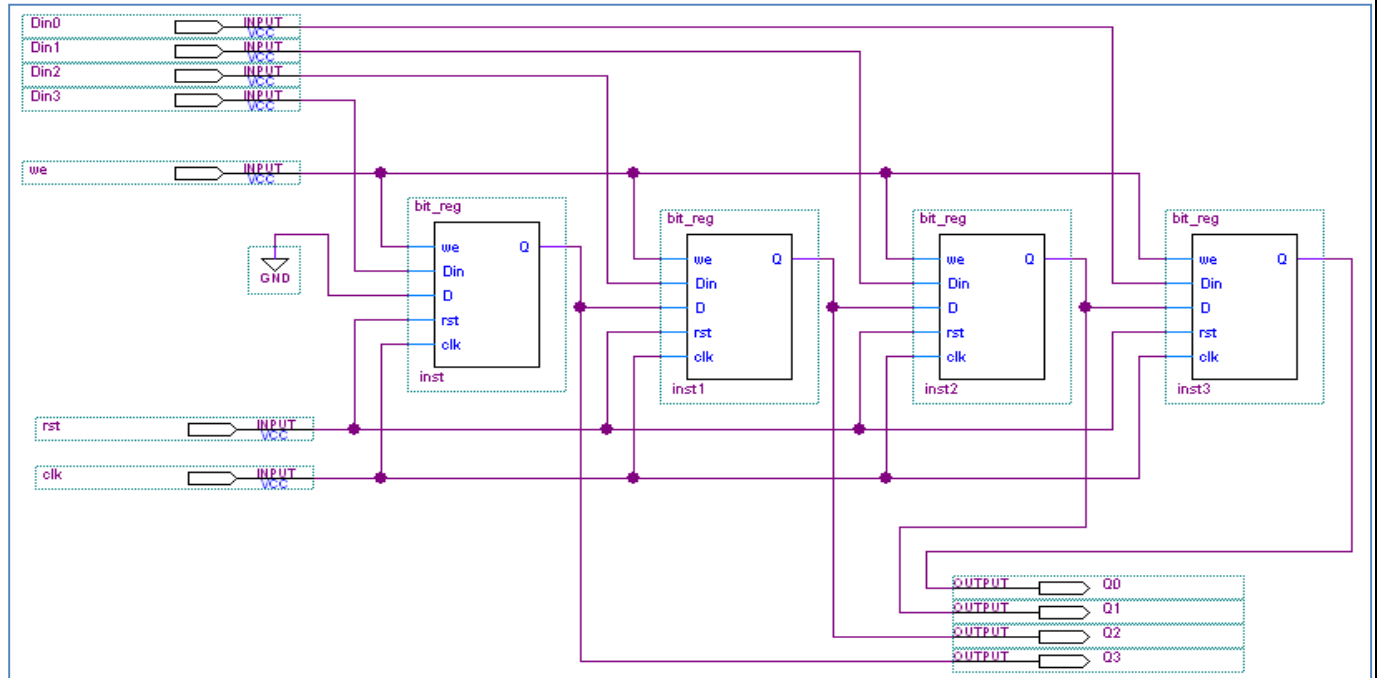


Figure 3: Schematic diagram of a 4-bit Shift Right Register with synchronous parallel input

```

LIBRARY IEEE;
use IEEE.STD_LOGIC_1164.ALL;

ENTITY sr_reg4 IS
PORT (      Din      : in   std_logic_vector(3 downto 0);
          rst,clk,we  : in   std_logic;
          Q           : out  std_logic_vector(3 downto 0));
END sr_reg4;

ARCHITECTURE beh OF sr_reg4 IS


COMPONENT bit_reg
PORT (      we, Din, D, rst, clk  : in   std_logic;
          Q           : out  std_logic );
END component;
:
: - complete this program for Figure 3.

```

```
1  LIBRARY IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  ENTITY sr_reg4 IS
5  PORT ( Din      : in    std_logic_vector(3 downto 0);
6        rst,clk,we : in    std_logic;
7        Q        : out   std_logic_vector(3 downto 0) );
8  END sr_reg4;
9
10 ARCHITECTURE beh OF sr_reg4 IS
11
12 COMPONENT bit_reg
13 PORT ( we, Din, D, rst, clk : in    std_logic;
14       Q                : out   std_logic );
15 END component;
16
17 SIGNAL x : STD_LOGIC_VECTOR(3 DOWNT0 0);
18
19 begin
20
21 STAGE1: bit_reg PORT MAP (we,Din(0),x(1),rst,clk,x(0));
22 STAGE2: bit_reg PORT MAP (we,Din(1),x(2),rst,clk,x(1));
23 STAGE3: bit_reg PORT MAP (we,Din(2),x(3),rst,clk,x(2));
24 STAGE4: bit_reg PORT MAP (we,Din(3),'0',rst,clk,x(3));
25
26 Q <= x;
27
28 end beh;
```

(c) Attach the following figures to prove your project is successful.

 
1. Successful compilation report that shows your Project Folder (Name & Matric) and Project Name




All screenshots must clearly show your project folder and active projects (in the red boxes).

Waveform setting :
End Time : 800ns
Grid Size : 10ns
Waveform and IO as shown in screenshot

2. Waveform

 

3. RTL (optional)

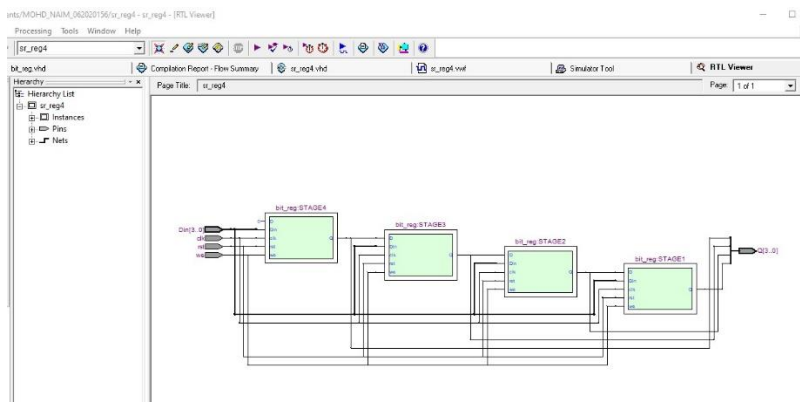

QUESTION 2

The following VHDL program for an ALU has several errors detected in them when compiled using the Altera Quartus II software. Create a 3-column table (as shown below) to

1. Identify the lines containing the error,
2. Brief explanation about the error
3. Proposed corrected line

```
Line
1  library ieee;
2  use ieee.std_logic_1164_all;
3  use ieee.std_logic_arith_all;
4  use ieee.std_logic_unsigned_all;
5
6  entity test_alu4 is
7  port (  inA, inB, outC      : in   std_logic_vector(3 downto 0);
8         Sel                 : in   std_logic_vector(1 downto 0);
9         Carry, Bigger       : out  std_logic);
10 end test_alu4;
11
12 architecture labtest of test_alu4 is
13     temp : std_logic_vector(4 downto 0);
14 begin
15     process (inA, inB, sel, temp)
16         Bigger <= "0";
17         Case sel is
18             When "00" =>
19                 temp <= ("0" & inA) + ("0" & inB);
20                 outC <= temp(4 downto 1);
21                 Carry <= temp(0);
22             When "01" =>
23                 If inA => inB then
24                     outC <= inA - inB;
25                     Bigger <= "0";
26                 Else
27                     outC <= inB - inA;
28                     Bigger <= "1";
29             When "10" =>
30                 outC <= inA and inB;
31             When "others" =>
32                 outC <= inA or inB;
33             end case;
34         end process
35 end test_alu4;
```

Line No.	Brief explanation on error	Propose correction
2,3,4	Underscore before "all" Correct is (use "•")	~1164.all / ~arith.all / ~unsigned.all
7	OutC is not mode in	Create new line in entity declaration → outC : out std_logic_vector(3 downto 0);
10	Wrong entity name	end test_alu4;
13	No 'signal' vhdl keyword	signal temp : std_logic_vector(4 downto 0);
15	VHDL keyword "begin" for process is missing	Create new line → begin (before current line 16)
16,19,25,28	1-bit use single quotation	'0' or '1'
28	VHDLkeyword "end if" is missing	Create new line → end if;
34	“;” missing	end process;

***** GOOD ***** LUCK *****