

**PUSAT PENGAJIAN DIPLOMA
UNIVERSITI MALAYSIA PERLIS**

Tutorial 3

DKT214 – Electronic Circuits; Semester 1 2017/2018

1. What is the main purpose of an instrumentation amplifier and what are three of its key characteristics?
2. What components are needed to construct a basic instrumentation amplifier?
3. Refer to Figure 3.1, determine:
 - (a) Voltage gains of op-amp A1 and A2
 - (b) The overall voltage gain.
 - (c) The output voltage if $V_{in1} = 3 \text{ mV}$, $V_{in2} = 15 \text{ mV}$.

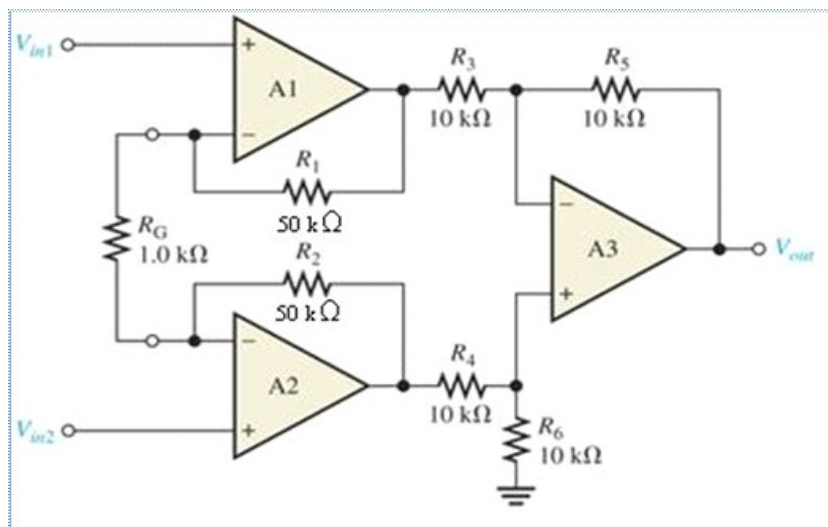


Figure 3.1

4. Calculate the voltage gain for the instrumentation amplifier in Figure 3.2.

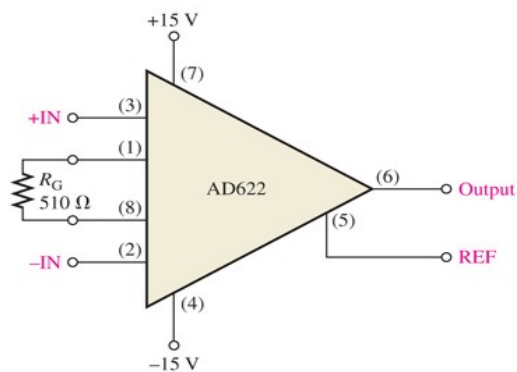


Figure 3.2

5. Determine the total gain of the 3656KG isolation amplifier in Figure 3.3.

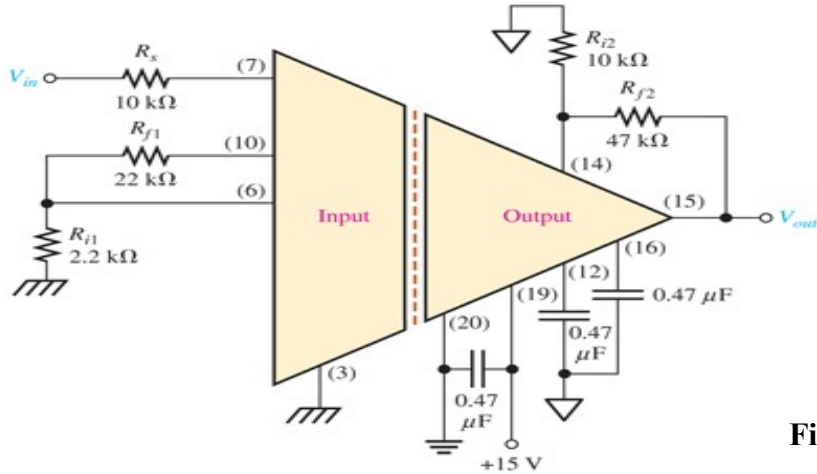


Figure 3.3

6. In what types of applications are isolation amplifiers used?
7. What are the two stages in a typical isolation amplifier and what is the purpose of having two stages?
8. What purpose does the diode or transistor perform in the feedback loop of a log amplifier.
9. Why is the output of a log amplifier limited to about 0.7 V?
10. What are the factors that determine the output voltage of a basic log amplifier?
11. In terms of implementation, how does a basic antilog amplifier differ from a basic log amplifier?
12. Determine the output voltage for the amplifier in Figure 3.4. Assume $I_R = 50 \text{ nA}$.

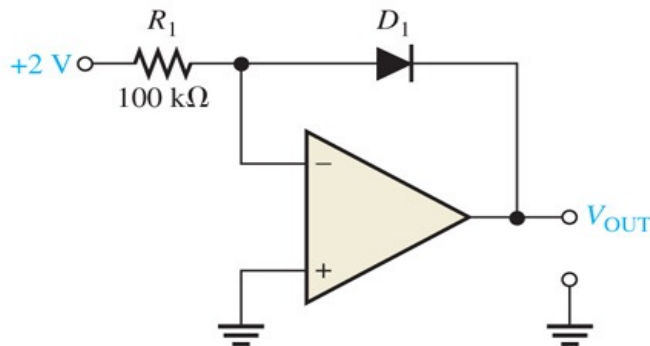


Figure 3.4

13. Determine the output voltage for the log amplifier in Figure 3.5. Assume $I_{EBO} = 60 \text{ nA}$.

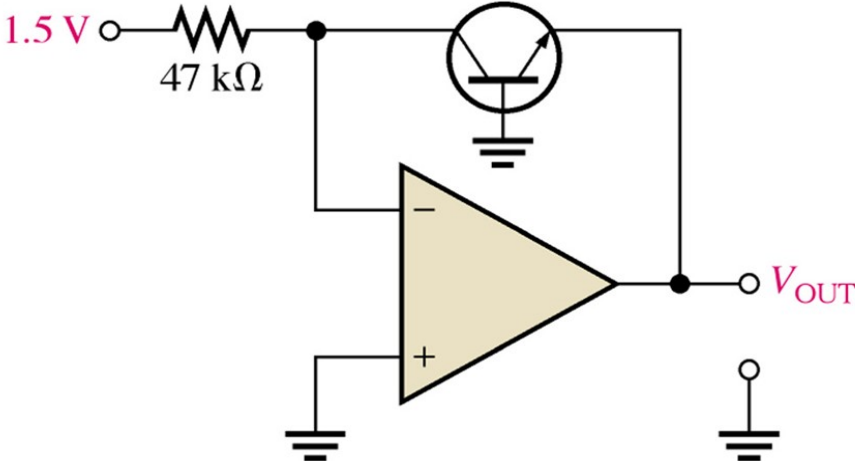


Figure 3.5

14. Determine the output for the antilog amplifier in Figure 3.6. Assume $I_{EBO} = 60 \text{ nA}$.

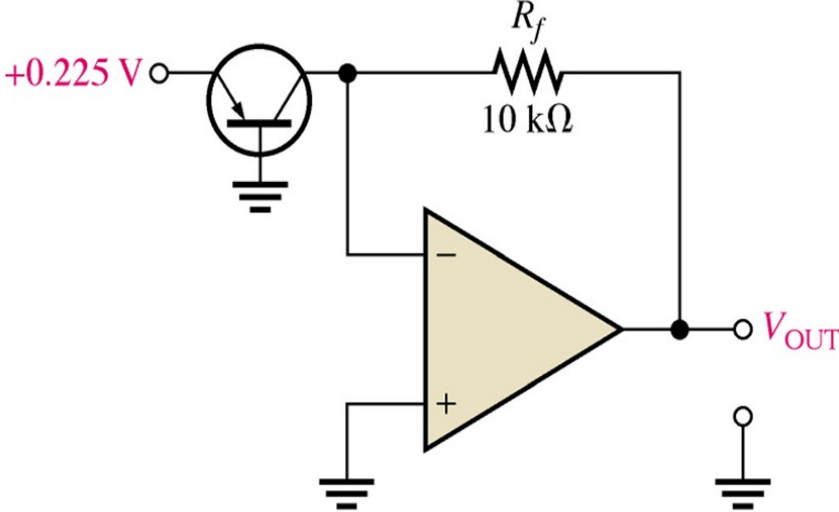


Figure 3.6