

PAPER 1
(CO1, C4)

This part has **TWO (2)** questions. Answer **ALL** questions. (30 marks).

Question 1

Figure 1 shows a combination of flip-flops and latch. Draw the output waveform of signals W , X , Y and Z in **Appendix I**. Assume that all the output values are initially at 0.

(15 Marks)

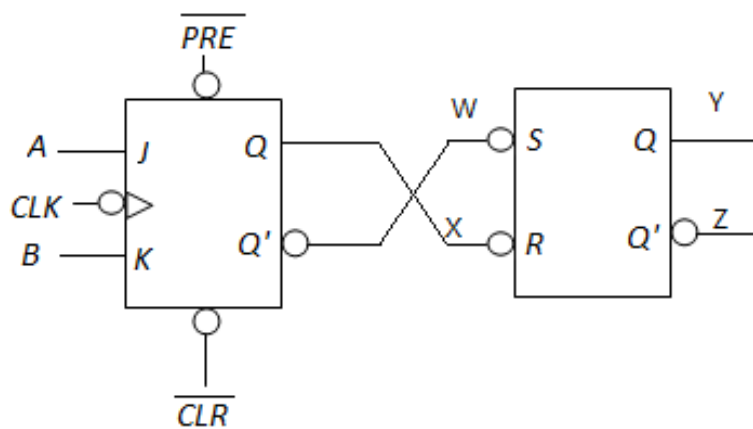


Figure 1

Question 2

Sketch the logic diagram of 4-bit SIPO shift register using D flip-flops. Then, develop the timing diagram of 4-bit SIPO shift register using D flip flop. Let the input data $Q_3Q_2Q_1Q_0=0111$. Complete the outputs for Q_3 , Q_2 , Q_1 and Q_0 for four(4) clock cycles. Assume that the register initially contains all 1's.

Complete your answer in **Appendix 2**.

(15 marks)

Appendix 1

Question 1

Angka Giliran: _____

Nama: _____

ID: _____

