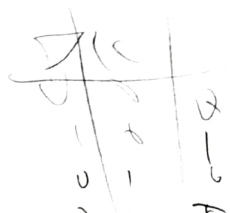


SULIT

Question 1

- (a) Latches and flip-flops are the basic elements for storing information. Describe the differences between latch and flip-flops. (4 Marks)
- (b) The master-slave flip-flops was developed to make the synchronous operation more predictable. Describe this master-slave flip-flops operation. (5 Marks)
- (c) With aid of appropriate register diagrams, draw the **FOUR (4)** modes of shift operation on a 3-bit shift register. (4 Marks)
- (d) Determine all the Q output waveforms for 4-bit shift register when the inputs are as shown in Figure 1. Assume that the register is initially LOW and negative triggered CLOCK input. (5 Marks)



Question 2

Counters are flip-flop registers that can change their data values known as “binary states” or “states”. Counters can either operate synchronously or asynchronously with a common clock pulse.

- (a) Construct a modulus-11 asynchronous counter with a straight binary sequence from 0000 through 1010 using JK flip-flop. (4 Marks)
- (b) Determine the counter sequence in **Figure 2**. Assume that Q_2 , Q_1 and Q_0 are initially at 0. (6 Marks)


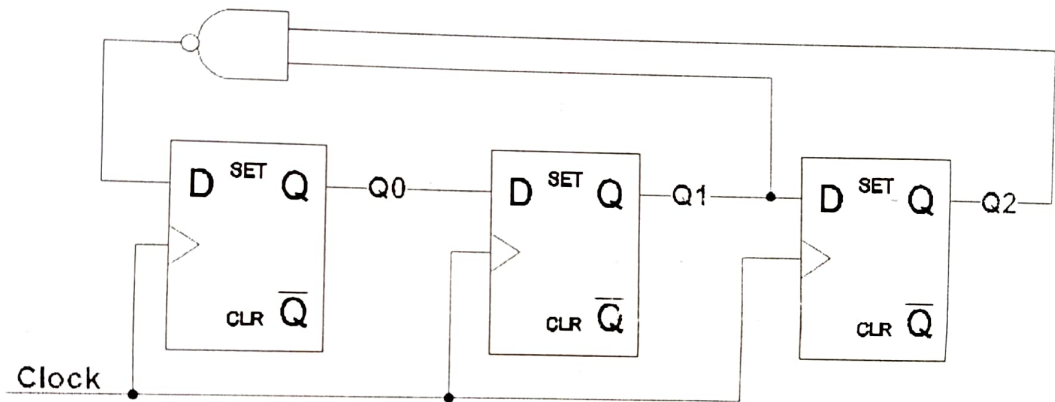


Figure 2

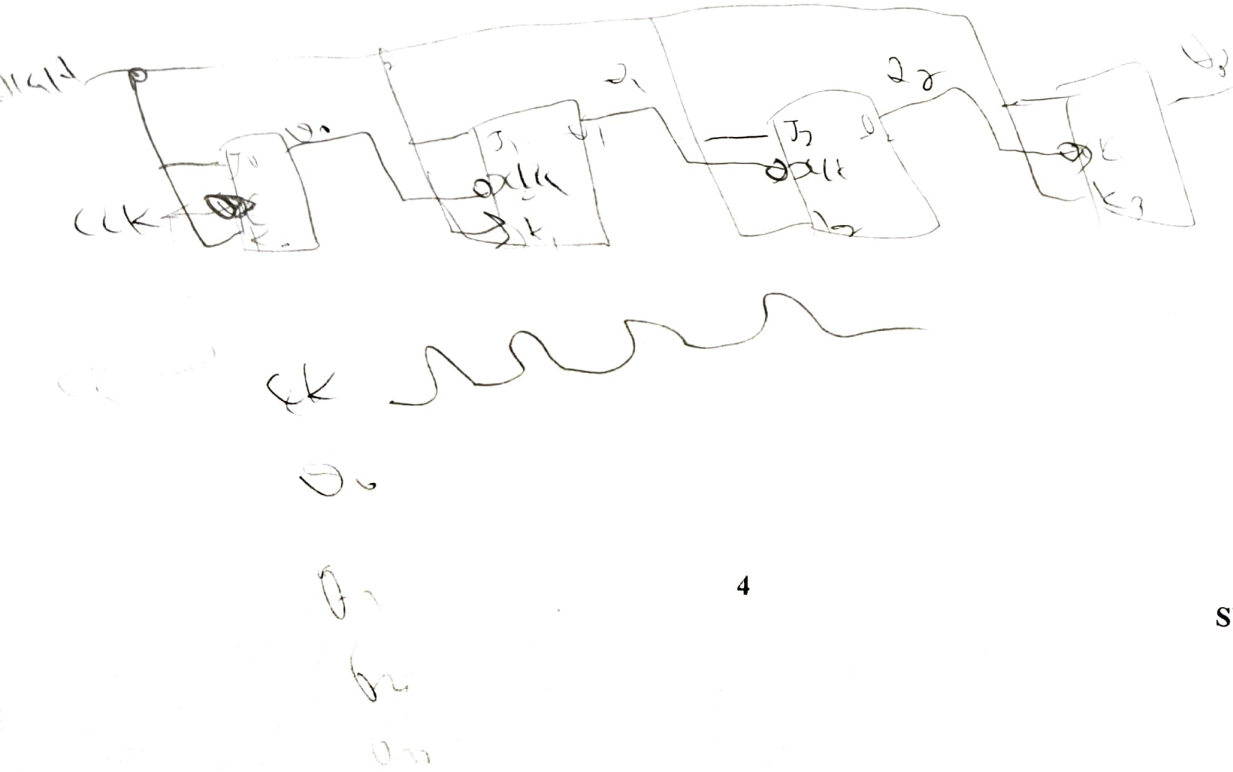

Question 3

Figure 3 shows a sequential circuit.

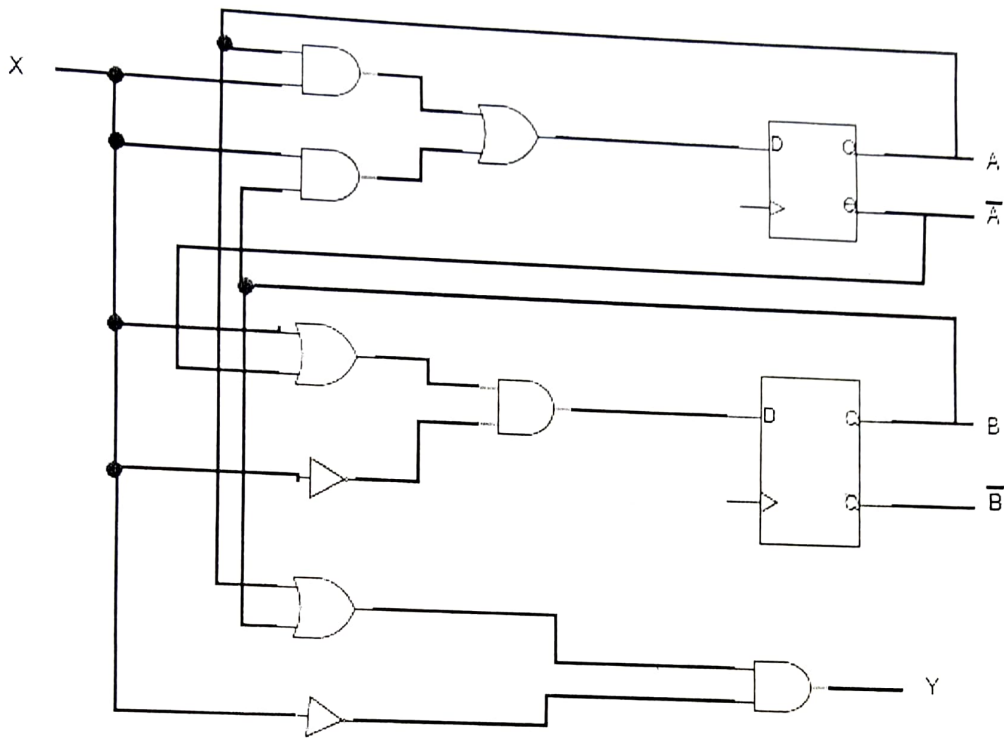


Figure 3

- (a) Derive the state table which includes present state, input X, next state and output Y. (8 Marks)
- (b) Based on the state table derived in (i), draw the state machine model. (4 Marks)