
UNIVERSITI MALAYSIA PERLIS

OPEN BOOK TEST (ONLINE)
Semester Pertama
Sidang Akademik 2021/2022

Oktober 2021

**NDJ20103 – Digital System II /
DKT212 – Digital System II
[Sistem Digit II]**

Paper 1

Masa : 35 minit

Please make sure that this question paper has **TWO (2)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **DUA (2)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This paper has **TWO (2)** questions. Answer **ALL** questions. (15 Marks)

*[Kertas ini mengandungi **DUA (2)** soalan. Jawab **SEMUA** soalan. (15 Markah)]*

Question 1

Give your complete answer in **Appendix 1**.

- a) Draw an asynchronous active-HIGH JK flip flop block diagram with a negative edge triggering clock pulse.
(2 marks)

- b) Complete the output waveform for Q according to the flip flop on **Question 1(a)**. Let input J & K set to 1. Assume the output for Q initially 0.
(3 marks)

Question 2

Give your complete answer in **Appendix 2**.

- a) Draw a master-slave flip flop block diagram. Let the master as a D flip flop while the slaves as a JK flip flop.
(4 marks)

- b) From the master-slave block diagram **on Question 2(a)**, complete the timing diagram in **Appendix 2**. Let assume the output for Q_{Master} and Q_{Slave} initially 0.
(6 marks)

-000000-

Appendix 1


Nama: _____

ID: _____

Question 1

a)

b)

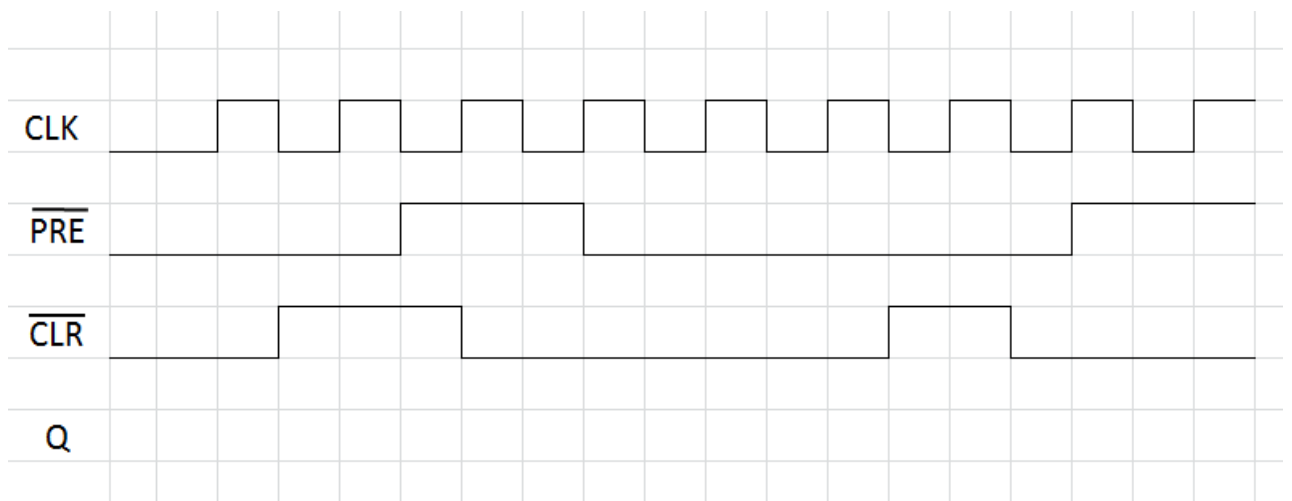

Appendix 2

Nama: _____

ID: _____

Question 2

a)

b)

