
UNIVERSITI MALAYSIA PERLIS

OPEN BOOK TEST (ONLINE)
Semester Pertama
Sidang Akademik 2021/2022

Okttober 2021

**NDJ20103 – Digital System II /
DKT212 – Digital System II
[Sistem Digit II]**

Paper 2

Masa : 45 minit

Please make sure that this question paper has **TWO (2)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **DUA (2)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*


This paper has **ONE (1)** question. Answer **ALL** questions. (22 Marks)
*[Kertas ini mengandungi **SATU (1)** soalan. Jawab **SEMUA** soalan. (22 Markah)]*

Question 1

Synthesize the sequential diagram below.

(22 marks)

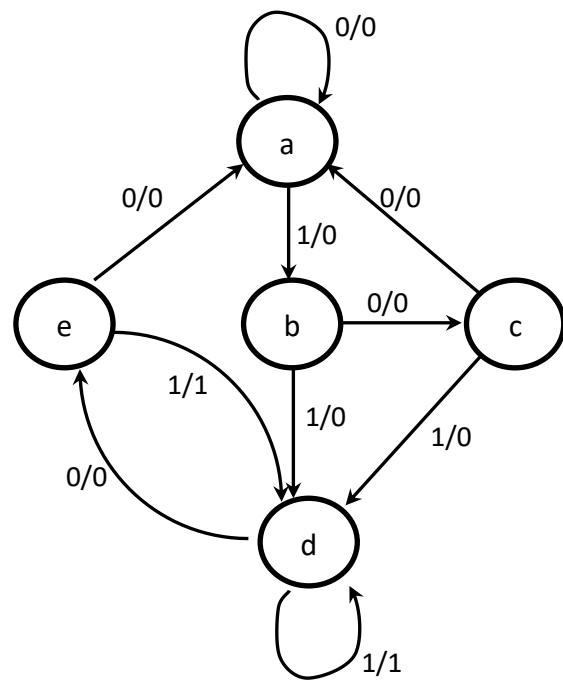(remarks: by referring your last digit matric id, the odd number will synthesize using SRFF and the even number will synthesize using JKFF)



-oooOoo-