

SULIT

UNIVERSITI MALAYSIA PERLIS

Peperiksaan Semester Kedua
Sidang Akademik 2007/2008

21 April 2008

DMT 241 – Introduction To Integrated Circuit Layout
[Pengantar Bentangan Litar Terkamir]

Masa : 3 Jam

Please make sure that this question paper has **ELEVEN (11)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **SEBELAS (11)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This question paper has **SIX** questions. Answer any **FIVE** questions only.
*[Kertas soalan ini mengandungi **ENAM** soalan. Jawab mana-mana **LIMA** soalan sahaja.]*

SULIT

Question 1**[Soalan 1]**

- (a) List **TWO (2)** advantages and disadvantages of Application Specific Integrated Circuits system.

[4 marks]*[Senaraikan DUA (2) kelebihan dan kekurangan sistem litar terkamir beraplikasi spesifik.]***[4 markah]**

- (b) List **THREE (3)** differences between Full Custom design and Field-Programmer Gate Arrays design.

[6 marks]*[Senaraikan TIGA (3) perbezaan diantara rekabentuk binaan penuh dan rekabentuk 'Field-Programmer Gate Arrays'.]***[6 markah]**

- (c) State **THREE (3)** operation regions for transistor.

[3 marks]*[Nyatakan TIGA (3) kawasan operasi bagi transistor.]***[3 markah]**

- (d) An NMOS transistor is in a $0.3 \mu\text{m}$ technology with $W/L = 5/2$. The gate oxide thickness for this process is 100 \AA , the mobility of electrons is $350 \text{ cm}^2/\text{V.S}$ and the threshold voltage is 0.7 V . Assume V_{dd} is equal to 5 V . Determine the operation region of NMOS if the value I_d across source to drain is 200 mA .

[7 marks]*[Satu transistor jenis NMOS berteknologi $0.35 \mu\text{m}$ dengan $W/L = 5/2$. Ketebalan get oksida bagi proses ini adalah 100 \AA , pergerakkan elektron adalah $350 \text{ cm}^2/\text{V.S}$ dan voltan ambang adalah 0.7 V . Andaikan V_{dd} bersamaan 5 V . Tentukan kawasan operasi bagi NMOS sekiranya nilai I_d merentasi punca ke salir adalah 200 mA .]***[7 markah]**

Question 2*{Soalan 2}*

- (a) Briefly explain:

[Terangkan secara ringkas:]

- (i) Transient Analysis

*[Analisa transien]***[2 marks]***[2 markah]*

- (ii) DC Analysis

*[Analisa AT]***[2 marks]***[2 markah]*

- (iii) AC Analysis

*[Analisa AU]***[2 marks]***[2 markah]*

- (b) Given $Q = A\bar{B} + \bar{A}B$:

[Diberikan $Q = A\bar{B} + \bar{A}B$:]

- (i) Write subckt netlist.

*[Tuliskan netlist subckt.]***[7 marks]***[7 markah]*

- (ii) Write a test-bench netlist using Piecewise Linear (PWL) source as an input signal.

[4 marks]*[Tuliskan netlist testbench menggunakan isyarat masukan Piecewise Linear (PWL) sebagai isyarat masukan.]**[4 markah]*

- (c) Refer to **Figure 2**, write the stimulus using PULSE as an input source.

[3 marks]*[Rujuk kepada Rajah 2, tuliskan 'stimulus' menggunakan 'PULSE' sebagai sumber masukan.]**[3 markah]**....4/-*

 


Figure 2

Rajah 2

Question 3**[Soalan 3]**

- (a) A 2:1 multiplexer can be developed by cascading THREE (3) 2-input NAND gates.

[Satu pemultipleks 2:1 boleh dibina dengan melatakan TIGA (3) gerak TAK DAN 2-masukan.]

- (i) Sketch a block diagram for the 2:1 multiplexer. [6 marks]
[Lakarkan satu gambarajah blok untuk 2:1 pemultipleks.] [6 markah]

- (ii) Sketch the CMOS transistor level schematic circuit. [10 marks]
[Lakarkan litar skematik aras transistor CMOS.] [10 markah]

- (b) Design a 4:1 multiplexer by using the 2:1 multiplexer block diagram in part a (i). [4 marks]

[Rekabentukkan satu pemmultipleks 4:1 dengan menggunakan gambarajah blok pemmultipleks 2:1 daripada bahagian a(i).] [4 markah]

Question 4**{Soalan 4}**

- (a) Sketch the corresponding transistor level schematic circuit in **Figure 4a** using:

[*Lakarkan skematik aras transistor berpandukan Rajah 4a dengan menggunakan:*]

(i) CMOS [8 marks]
[*CMOS*] [8 markah]

(ii) Pseudo NMOS [2 marks]
[*Pseudo NMOS*] [2 markah]

- (b) Refer to **Figure 4b**. Complete the CMOS circuit based on PUN configuration.

[8 marks]

[*Rujuk kepada Rajah 4b. Lengkapkan litar CMOS berdasarkan konfigurasi PUN.*]

[8 markah]

- (c) Write the Boolean equation based on answer in part b.

[2 marks]

[*Tuliskan persamaan Boolean berdasarkan jawapan dalam bahagian b.*]

[2 markah]

 


Figure 4a

 
Rajah 4a

Figure 4b

Rajah 4b

Question 5**{Soalan 5}**

- (a) Refer to the layout shown in **Figure 5a**.

[Rujuk kepada bentangan yang di tunjukkan di Rajah 5a.]

- (i) Sketch the stick diagram.

[Lakarkan rajah ranting.]

[3 marks]

[3 markah]

- (ii) Sketch the corresponding transistor level schematic circuit.

[Lakarkan litar skematik aras transistor yang sepadan.]

[7 marks]

[7 markah]

- (iii) Derive the Boolean equation for the circuit.

[Terbitkan persamaan Boolean bagi litar tersebut.]

[2 marks]

[2 markah]

- (b) Refer to the circuit in **Figure 5b**:

[Rujuk kepada litar di Rajah 5b:]

- (i) Derive the Boolean equation.

[Terbitkan persamaan Boolean.]

[2marks]


[2 markah]

- (ii) Write the truth table for the circuit.

[Tuliskan jadual kebenaran bagi litar tersebut.]

[6marks]

[6 markah]

 

Legend

Polysilicon

P-diffusion

N-well

Metal 1

N-diffusion

Contact

Figure 5a

Rajah 5a

....10/-

 


Figure 5b

Rajak 5b

Question 6*[Soalan 6]*

- (a) Refer to **Figure 6**:

[Rujuk kepada Rajah 6.]


- (i) Sketch the Euler Path for the circuit.

[4 marks]*[Lakarkan Laluan Euler bagi litar tersebut.]***[4 markah]**

- (ii) Sketch the stick diagram based on your answer in a(i).

[4 marks]*[Lakarkan rajah ranting berdasarkan jawapan dalam a(i).]***[4 markah]**

- (iii) Draw the layout based on $0.35 \mu\text{m}$ technology. Label the width and spacing.

 [12 marks]*[Lukiskan bentangan berdasarkan teknologi $0.35 \mu\text{m}$. Labelkan lebar dan jarak.]***[12 markah]****Figure 6***Rajah 6*