
UNIVERSITI MALAYSIA PERLIS

Peperiksaan Semester Kedua
Sidang Akademik 2015/2016

Mac 2016

DMT241 – Introduction To Integrated Circuit Layout
[Pengenalan Kepada Pengantar Bentangan Litar Terkamir]

Masa: 3 jam

Please make sure that this question paper has **FOURTEEN (14)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **EMPAT BELAS (14)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This question paper has **SIX** questions. Answer **any FIVE** questions. Each question contributes 20 marks.

*[Kertas soalan ini mengandungi **ENAM** soalan. Jawab mana-mana **LIMA** soalan. Markah bagi tiap-tiap soalan adalah 20 markah.]*

Appendix I is given for **Question 1(c)(iv)**.

[Lampiran I diberi untuk Soalan 1(c)(iv).]

Question 1**[Soalan 1]**

- (a) First Integrated Circuit (IC) was invented by Jack Kilby from Texas Instruments in the year of 2000.
[Litar Bersepadu (IC) pertama telah direka oleh Jack Kilby dari Texas Instruments pada tahun 2000.]
- (i) Define IC.
[Takrifkan IC.]
(2 Marks / Markah)
- (ii) Name **TWO (2)** types of materials used to build transistor and the circuit inside an IC.
[Namakan DUA (2) jenis bahan-bahan yang digunakan bagi membina transistor dan litar di dalam IC.]
(1 Mark / Markah)
- (iii) Explain **TWO (2)** applications of an IC.
[Terangkan DUA (2) aplikasi-aplikasi sebuah IC.]
(2 Marks / Markah)
- (b) Most of modern IC's today used Complementary Metal Oxide Semiconductor (CMOS) technology as their basic technology.
[Kebanyakan IC moden hari ini menggunakan teknologi Pelengkap Separa Pengalir-Oksida-Logam (CMOS) sebagai teknologi asas mereka.]
- (i) Name **TWO (2)** types of devices in CMOS.
[Namakan dua jenis peranti dalam CMOS.]
(1 Mark / Markah)
- (ii) Define CMOS technology.
[Takrifkan teknologi CMOS.]
(3 Marks / Markah)

....3/-

(c) Refer to netlist in **Figure 1a**.

[Rujuk netlist dalam Rajah 1a.]

(i) Sketch the transistor level schematic.

[Lakarkan litar skematik aras transistor.]

(4 Marks / Markah)

(ii) Identify the Boolean equation.

[Kenalpasti persamaan Boolean.]

(1 Mark / Markah)

(iii) Write the testbench netlist using Piecewise Linear (PWL) source as the input signal in **Figure 1b** in **Appendix I**. Given $VDD = 5V$, $GND = 0V$, time delay (t_d) = rise time (t_r) = fall time (t_f) = 1ns.

[Tuliskan "testbench netlist" menggunakan sumber Lelurus Cebisan (PWL) sebagai isyarat input di Rajah 1b. Diberikan $VDD = 5V$, $GND = 0V$, lengah masa (t_d) = masa naik (t_r) = masa jatuh (t_f) = 1ns.]

(4 Marks / Markah)

(iv) Sketch the output waveform, OUT in **Appendix I**.

[Lakarkan gelombang keluaran, OUT dalam Lampiran I.]

(2 Marks / Markah)

<i>.subckt QUESTION1</i>							
	A	B	C	D	OUT		
MP1	N1	A	VDD	VDD	p	L=0.4u	W=1u
MP2	OUT	B	N1	VDD	p	L=0.4u	W=1u
MP3	OUT	C	N1	VDD	p	L=0.4u	W=1u
MP4	OUT	D	N1	VDD	p	L=0.4u	W=1u
MN1	OUT	A	GND	GND	n	L=0.4u	W=1u
MN2	OUT	B	N2	GND	n	L=0.4u	W=1u
MN3	N2	C	N3	GND	n	L=0.4u	W=1u
MN4	N3	D	GND	GND	n	L=0.4u	W=1u

.ends QUESTION1

Figure 1a

[Rajah 1a]

Question 2*[Soalan 2]*

- (a) The chip complexity has increased by a factor of ~ 1000 since its first introduction.
[Kerumitan cip telah bertambah dengan satu faktor ~ 1000 sejak pengenalan pertamanya.]

- (i) List **TWO (2)** industry trends of an Integrated Circuit (IC).
[Senaraikan DUA (2) aliran industri sebuah Litar Bersepadu (IC).]

(2 Marks / Markah)

- (ii) Briefly explain the evolution of an IC in **Figure 2a**.
[Terangkan secara ringkas evolusi IC dalam Rajah 2a.]

(2 Marks / Markah)

 


Figure 2a
[Rajah 2a]

- (iii) List **FOUR (4)** classification of integration level of chip with its number of transistors.

[Senaraikan EMPAT (4) pengkelasan tahap integrasi cip beserta dengan jumlah transistornya.]
(2 Marks / Markah)

....5/-

- (b) Based on the equation below;
 [Berdasarkan persamaan di bawah;]

$$Z = \overline{P + (\overline{QR})}$$

- (i) simplified the equation by using De Morgan's Theorem.
 [permudahkan persamaan tersebut dengan menggunakan Teorem De Morgan.]
 (2 Marks / Markah)
- (ii) state the number of transistors used in (b)(i).
 [nyatakan jumlah transistor yang digunakan dalam (b)(i).]
 (1 Mark / Markah)
- (iii) sketch the transistor level schematic in (b)(ii).
 [takarkan litar skematik aras transistor dalam (b)(ii).]
 (4 Marks / Markah)
- (iv) write the netlist body for answer for (b)(iii).
 [tuliskan badan netlist untuk (b)(iii).]
 (4 Marks / Markah)
- (v) write a simulator netlist using PULSE source as in **Figure 2b**. Given $V_1 = 0V$, $V_2 = 5V$, time delay (t_d) = 0s, rise time (t_r) = fall time (t_f) = 1s.
 [tuliskan netlist pensimulasi menggunakan sumber PULSE seperti di **Rajah 2b**. Diberikan $V_1 = 0V$, $V_2 = 5V$, lengah masa (t_d) = 0s, masa naik (t_r) = masa jatuh (t_f) = 1s.]
 (3 Marks / Markah)

 


Figure 2b
 [Rajah 2b]

Question 3**[Soalan 3]**

- (a) Differentiate NMOS and PMOS transistor in term of;
[Bezakan transistor NMOS dan PMOS berdasarkan terma;]
- (i) structure.
[struktur.] (2 Marks / Markah)
- (ii) transistor as a switch.
[transistor sebagai suatu suis.] (4 Marks / Markah)
- (b) State **THREE (3)** operation regions for an NMOS transistor.
[Nyatakan **TIGA (3)** keadaan operasi bagi sebuah transistor NMOS.] (3 Marks / Markah)
- (c) With the aid of diagram, briefly explain answer in (b).
[Dengan bantuan gambarajah, terangkan secara ringkas jawapan di (b).] (4 Marks / Markah)
- (d) The NMOS transistor is designed with width/length = 8/2, $t_{ox} = 100\text{\AA}$, $\mu_n = 350\text{ cm}^2/\text{V.S}$ and $V_{TH} = 0.7\text{V}$.
[Transistor NMOS direka bentuk dengan kelebaran/panjang = 8/2, $t_{ox} = 100\text{\AA}$, $\mu_n = 350\text{ cm}^2/\text{V.S}$ dan $V_{TH} = 0.7\text{V}$.]
- (i) Calculate c_{ox} and β for the transistor.
[Kirakan c_{ox} dan β untuk transistor tersebut.] (3 Marks / Markah)
- (ii) Given the values of $V_{GS} = 0.3\text{V}$, 2.0V , 4.0V and 5V . Calculate the corresponding I_D values for each V_{GS} when the transistor is operating in the saturation region.
[Diberi nilai $V_{GS} = 0.3\text{V}$, 2.0V , 4.0V dan 5V . Hitungkan nilai-nilai I_D sepadan untuk setiap V_{GS} apabila transistor beroperasi dalam keadaan tepu.] (4 Marks / Markah)

Question 4*[Soalan 4]*

- (a) Layout verification is done to ensure that the logic design and physical design will function correctly as expected.

[Pengesahan bentangan dibuat untuk memastikan bahawa reka bentuk logik dan reka bentuk fizikal akan berfungsi seperti yang dijangka.]

- (i) Differentiate Design Rules Check (DRC) and Layout Versus Schematic (LVS).

[Bezakan Aturan Rekabentuk Memeriksa (DRC) dan Bentangan Lawan Skematik (LVS).]

(4 Marks / Markah)

- (ii) With the aid of diagram, sketch an example for DRC and LVS error.

[Dengan bantuan gambarajah, lakar satu contoh untuk ralat DRC and LVS.]

(2 Marks / Markah)

- (iii) Explain way to fix the error for answer in (a)(ii).

[Jelaskan cara membetulkan ralat untuk jawapan di (a)(ii).]

(2 Marks / Markah)

- (b) A Complementary Metal Oxide Semiconductor (CMOS) is a combination of Pull Down Network (PDN) and Pull Up Network (PUN). Based on **Figure 4**;

[Pelengkap Separa Pengalir-Oksida-Logam (CMOS) ialah satu kombinasi Rangkaian Tarik-Bawah (PDN) and Rangkaian Tarik-Naik (PUN). Berdasarkan Rajah 4:]

 


Figure 4
[Rajah 4]

....8/-

- (i) sketch the complete PUN for the schematic.
[lakarkan PUN lengkap untuk skematik tersebut.]
(5 Marks / Markah)
- (ii) identify the Boolean equation for the output, Z.
[kenalpasti persamaan Boolean untuk keluaran, Z.]
(1 Mark / Markah)
- (iii) sketch the Euler path for {B, A, E, D, C}.
[lakarkan laluan Euler bagi {B, A, E, D, C}.]
(1 Mark / Markah)
- (iv) sketch the stick diagram for the schematic.
[lakarkan gambarajah ranting bagi skematik tersebut.]
(5 Marks / Markah)

Question 5*[Soalan 5]*

- (a) Bipolar Junction Transistor (BJT) is an active semiconductor device formed by two p-n junctions.

[Persimpangan Dwikutub Transistor (BJT) ialah sebuah peranti semikonduktor aktif dibentuk oleh dua simpang p-n.]

- (i) With the aid of diagram, give TWO (2) configurations for this device.
[Dengan bantuan gambarajah, berikan DUA (2) konfigurasi-konfigurasi bagi peranti ini.]
 (2 Marks / Markah)

- (ii) Name the mechanism of particle diffusion for answer in (a)(i).
[Namakan mekanisme resapan zarah untuk jawapan di (a)(i).]
 (1 Mark / Markah)

- (iii) Figure 5(a) shows the operating region for an NPN transistor. State the operating region for the circled number.
[Rajah 5(a) menunjukkan kawasan operasi untuk satu transistor NPN. Nyatakan kawasan operasi bagi nombor yang dibulatkan.]
 (1 Mark / Markah)

- (iv) Briefly explain saturation region.
[Terangkan dengan ringkas kawasan ketepuan.]
 (2 Marks / Markah)


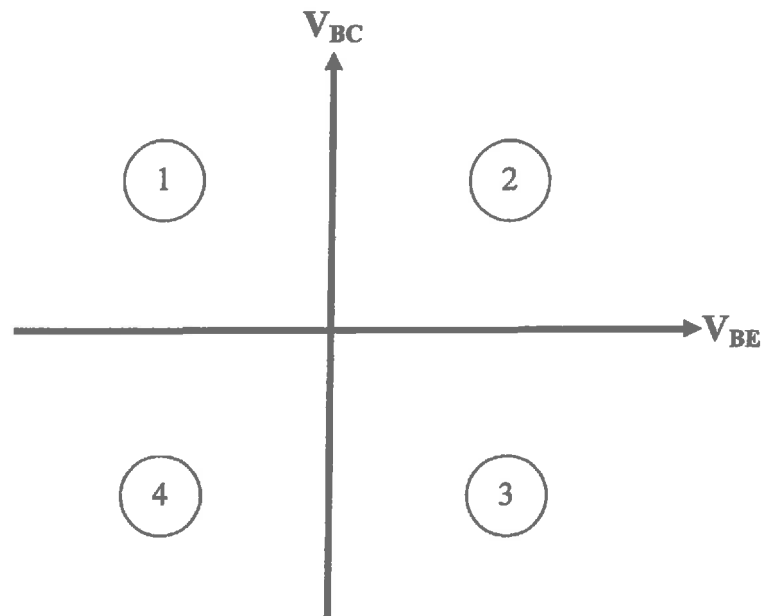


Figure 5(a)
[Rajah 5(a)]

....10/-

SULIT

 (b) Based on Figure 5(b):
[Berdasarkan Rajah 5(b):]



Legend:
[Petunjuk:]








- | | |
|---|---|
|  P-diffusion |  N-diffusion |
|  Polysilicon |  N-well |
|  Contact | |
|  Metal 1 | |
|  Metal 2 | |

Figure 5(b)
[Rajah 5(b)]

- (i) sketch the stick diagram.
[lakarkan gambarajah ranting.]
(2 Marks / Markah)
- (ii) sketch the corresponding transistor level schematic.
[lakarkan skematik aras transistor yang sepadan.]
(7 Marks / Markah)
- (iii) derive the Boolean equation for the schematic.
[terbitkan persamaan Boolean bagi skematik tersebut.]
(1 Mark / Markah)

 Question 6*[Soalan 6]*

- (a) An Application Specific Integrated Circuits (ASICs) is an integrated circuit customized for particular used in an IC. Explain **TWO (2)** advantages of ASICs.

[Litar Terkamil Beraplikasi Spesifik (ASICs) ialah satu litar bersepadu dibuat megikut perincian pesanan untuk digunakan dalam satu IC. Jelaskan DUA (2) kelebihan-kelebihan ASICs.]

(2 Marks / Markah)

- (b) Dynamic and static logic are two types of CMOS families. Differentiate dynamic and static logic.

[Logik dinamik dan statik ialah dua jenis keluarga-keluarga CMOS. Bezakan logik dinamik dan statik.]

(4 Marks / Markah)

- (c) Refer to **Figure 6**;

[Rujuk Rajah 6;]

 


Figure 6

[Rajah 6]

....13/-

SULIT

- (i) sketch the Euler path for the schematic.
[lakarkan laluan Euler bagi skematik tersebut.]
(1 Mark / Markah)
- (ii) sketch the stick diagram based on answer in (c)(i).
[lakarkan gambarajah ranting bagi jawapan di (c)(i).]
(4 Marks / Markah)
- (iii) draw the layout for (c)(ii) based on TSMC 0.35 μ m technology by using graph paper. Given length, $L = 2\lambda$ and width, $W = 5\lambda$ for the transistors. Label the width and spacing. (Use ratio $1\lambda : 2\text{mm}$).
[lukiskan bentangan untuk (c)(ii) berdasarkan teknologi TSMC 0.35 μ m dengan menggunakan kertas graf. Diberi panjang, $L = 2\lambda$ dan lebar, $W = 5\lambda$ bagi transistor-transistor tersebut. Labelkan lebar dan jarak. (Gunakan nisbah $1\lambda : 2\text{mm}$).]
(9 Marks / Markah)

Appendix I
[Lampiran I]

Question 1(c) (iv)
[Soalan 1(c) (iv)]

Angka Giliran: _____ No. Meja: _____

 


Figure 1b
[Rajah 1b]