

SULIT

UNIVERSITI MALAYSIA PERLIS

Peperiksaan Semester Pertama
Sidang Akademik 2017/2018

Oktober 2017

DMT 231 – Analogue Electronics
[Elektronik Analog]

Masa: 3 jam

Please make sure that this question paper has **FOURTEEN (14)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **EMPAT BELAS (14)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This question paper has **SIX (6)** questions. Answer any **FIVE (5)** question. Each question contribute 20 marks.

*[Kertas soalan ini mengandungi **ENAM (6)** soalan. Jawab mana-mana **LIMA (5)** soalan. Setiap soalan menyumbang 20 markah.]*

List of equation is given in **Appendix**.

*[Senarai persamaan-persamaan diberikan pada **Lampiran**.]*

SULIT

Question 1*[Soalan 1]*

- (a) Sketch and label the symbols of Bipolar Junction Transistor (BJT). Write the equation for each current flow.
[Lakar dan labelkan simbol-simbol bagi Transistor Simpangan Dwipolar (BJT). Tuliskan persamaan bagi setiap aliran arus.]
(4 Marks/ Markah)
- (b) BJT has 3 operation region which is cutoff, active and saturation. With the aid of diagram, explain **ALL** the operation regions.
[BJT mempunyai 3 kawasan operasi iaitu pemotongan, aktif dan tepu. Dengan bantuan gambarajah, terangkan SEMUA kawasan operasi.]
(6 Marks/ Markah)
- (c) Sketch and label the I-V characteristics curve for BJT.
[Lakar dan label lengkungan sifat IV bagi BJT.]
(3 Marks/ Markah)
- (d) Refer to **Figure 1**. Write the equation for;
[Rujuk Rajah 1. Tuliskan persamaan bagi:]
- (i) quiescent base current, I_{BQ} .
[arus tapak sepi, I_{BQ} .]
(1 Mark/ Markah)
- (ii) quiescent collector current, I_{CQ} .
[arus pemungut sepi, I_{CQ} .]
(1 Mark/ Markah)
- (iii) quiescent emitter, I_{EQ} .
[arus pemancar sepi, I_{EQ} .]
(1 Mark/ Markah)
- (iv) quiescent emitter-collector voltage, V_{CEQ} .
[voltan pemungut-pemancar sepi, V_{CEQ} .]
(1 Mark/ Markah)
- (v) sketch and label the DC load line for the circuit.
[lakar dan label garis beban AT untuk litar tersebut.]
(3 Marks/ Markah)

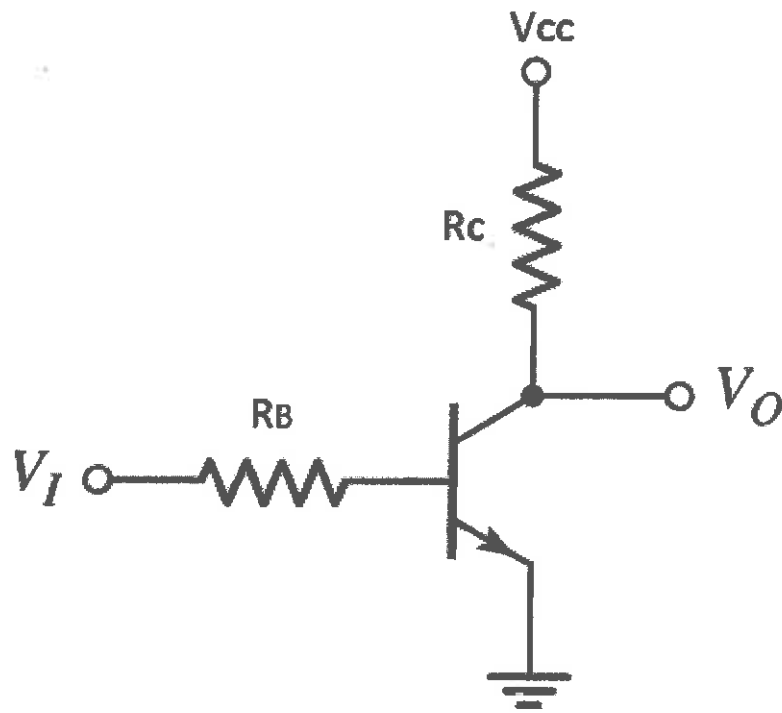


Figure 1
[Rajah 1]

Question 2*[Soalan 2]*

- (a) State **THREE (3)** basic types of BJT amplifiers.
[Nyatakan TIGA (3) jenis penguat BJT asas.] (1.5 Marks/ Markah)
- (b) **Figure 2** shows a common emitter amplifier circuit with $\beta = 100$, $V_{EB(on)} = 0.7$ V, $V_T = 26$ mV and $V_A = \infty$. Determine;
[Rajah 2 menunjukkan satu litar penguat pemancar sepunya dengan $\beta = 100$, $V_{EB(on)} = 0.7$ V, $V_T = 26$ mV dan $V_A = \infty$. Tentukan;]
- (i) Thevenin resistor, R_{TH} and Thevenin voltage, V_{TH} .
[perintang Thevenin, R_{TH} dan voltan Thevenin, V_{TH} .] (2.5 Marks/ Markah)
- (ii) base current, I_{BQ} .
[arus tapak, I_{BQ} .] (2 Marks/ Markah)
- (iii) collector current, I_{CQ} and emitter-collector voltage, V_{ECQ} .
[arus pemungut, I_{CQ} dan voltan pemancar-pemungut, V_{ECQ} .] (3 Marks/ Markah)
- (iv) transconductance, g_m .
[trankonduktan, g_m .] (1 Mark/ Markah)
- (v) diffusion resistance, r_π and output resistance, r_o .
[rintangan resapan, r_π dan rintangan keluaran, r_o .] (2 Marks/ Markah)
- (vi) sketch small signal equivalent circuit.
[lakarkan litar setara isyarat-kecil.] (5 Marks/ Markah)
- (vii) small-signal voltage gain, A_v .
[isyarat-kecil gandaan voltan, A_v .] (3 Marks/ Markah)

....5/-

SULIT

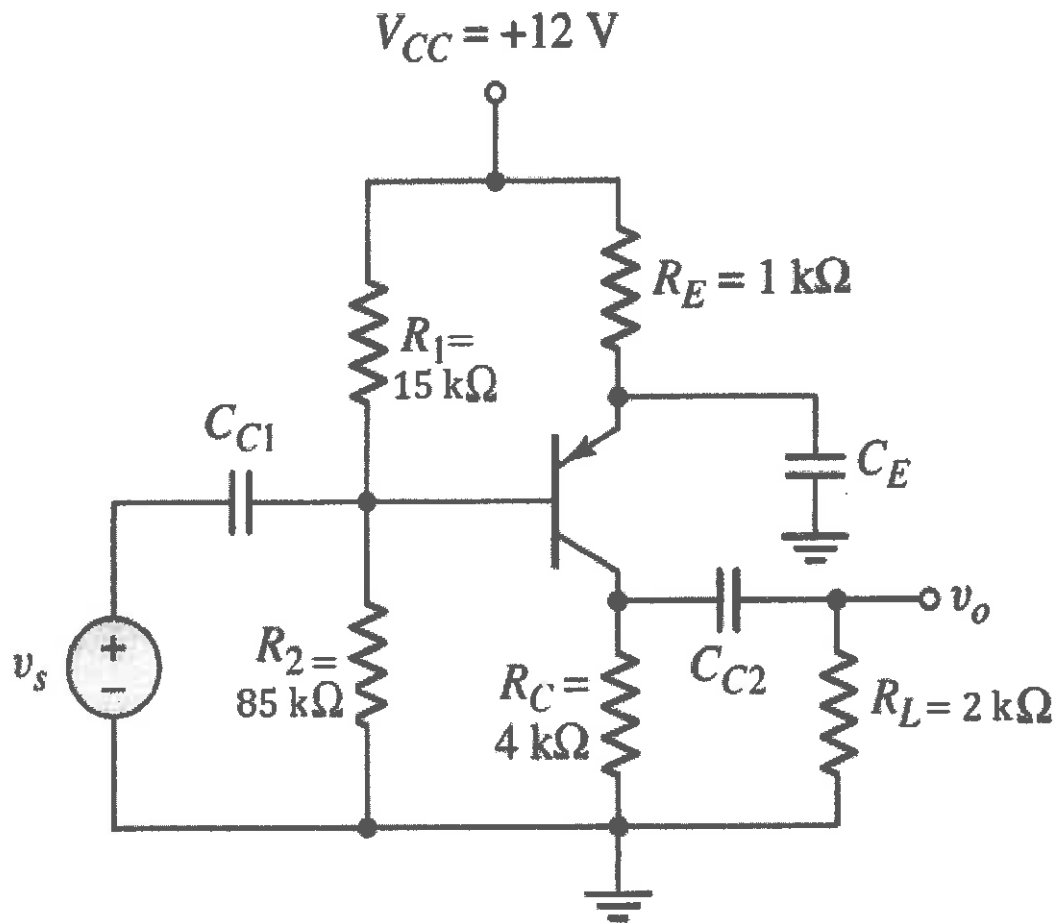


Figure 2
[Rajah 2]

Question 3*[Soalan 3]*

- (a) With the aid of diagram, explain the MOSFET operation.
[Dengan bantuan gambarajah, jelaskan operasi MOSFET.] (4 Marks/ Markah)
- (b) **Figure 3** show a MOSFET transistor with $K = 1 \text{ mA/V}^2$, $V_{TN} = 2\text{V}$ and $\lambda = 0$.
[Rajah 3 menunjukkan satu transistor MOSFET dengan $K = 1 \text{ mA/V}^2$, $V_{TN} = 2\text{V}$ dan $\lambda = 0$.]
- (i) Calculate gate voltage, V_G .
[Kirakan voltan pintu, V_G .] (2 Marks/ Markah)
- (ii) Calculate gate-source voltage, V_{GS} .
[Kirakan voltan pintu sumber, V_{GS} .] (3 Marks/ Markah)
- (iii) Calculate quiescent point (Q-point) values of I_{DQ} and V_{DSQ} .
[Kirakan nilai-nilai titik sepi (titik-Q) bagi I_{DQ} dan V_{DSQ} .] (4 Marks/ Markah)
- (iv) Calculate transconductance, g_m .
[Kirakan trankonduktan, g_m .] (1 Mark/ Markah)
- (v) Sketch the small- signal equivalent circuit for the circuit.
[Lakarkan litar setara isyarat-kecil untuk litar.] (4 Marks/ Markah)
- (vi) Calculate small-signal voltage gain $A_v = v_o / v_i$
[Kirakan gandaan voltan isyarat-kecil, $A_v = v_o / v_i$.] (2 Marks/ Markah)

...7/-

SULIT

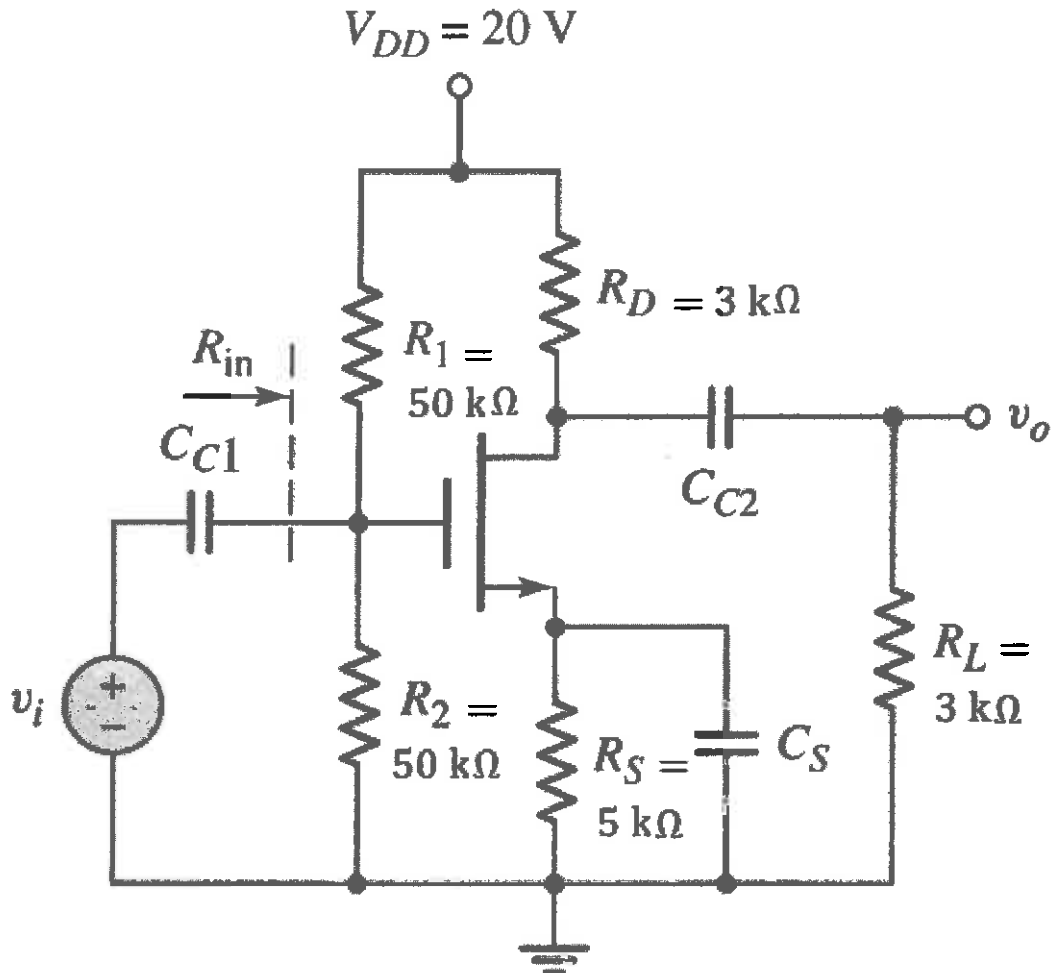


Figure 3
[Rajah 3]

Question 4*[Soalan 4]*

- (a) State and sketch **FOUR (4)** types of multistage amplifier configuration that you know.

[Nyata dan lakarkan EMPAT (4) jenis penguat berperingkat konfigurasi yang kamu tahu.]

(4 Marks/ Markah)

- (b) **Figure 4** shows a cascaded configuration as part of a multistage amplifier. The circuit elements transistor Q_1 and Q_2 are $\beta_1 = \beta_2 = 120$, $V_{BE(ON)} = 0.7 \text{ V}$ and $r_o = \infty$. Calculate;

[Rajah 4 menunjukkan konfigurasi terlantar sebagai sebahagian daripada penguat berbilang tahap. Elemen-elemen transistor Q_1 dan Q_2 adalah $\beta_1 = \beta_2 = 120$, $V_{BE(ON)} = 0.7 \text{ V}$ dan $r_o = \infty$. Kirakan;]

- (i) Thevenin resistor and voltage, R_{TH} and V_{TH} .

[voltan dan rintangan Thevenin, R_{TH} dan V_{TH} .]

(4 Marks/ Markah)

- (ii) transistor Q_1 quiescent current, I_{BQ1} , I_{CQ1} and I_{EQ1} .

[arus sepi transistor Q_1 , I_{BQ1} , I_{CQ1} dan I_{EQ1} .]

(3 Marks/ Markah)

- (iii) transistor Q_2 quiescent current, I_{EQ2} , I_{BQ2} and I_{CQ2} .

[arus sepi transistor Q_2 , I_{EQ2} , I_{BQ2} dan I_{CQ2} .]

(3 Marks/ Markah)

- (iv) transistor Q_1 and Q_2 quiescent voltage, V_{CEQ1} and V_{CEQ2} .

[voltan sepi transistor Q_1 dan Q_2 , V_{CEQ1} dan V_{CEQ2} .]

(2 Marks/ Markah)

- (c) Sketch small-signal equivalent circuit for circuit configuration shown in **Figure 4**.

[Lakarkan litar setara isyarat-kecil bagi konfigurasi litar yang ditunjukkan dalam Rajah 4.]

(4 Marks/ Markah)

....9/-

SULIT

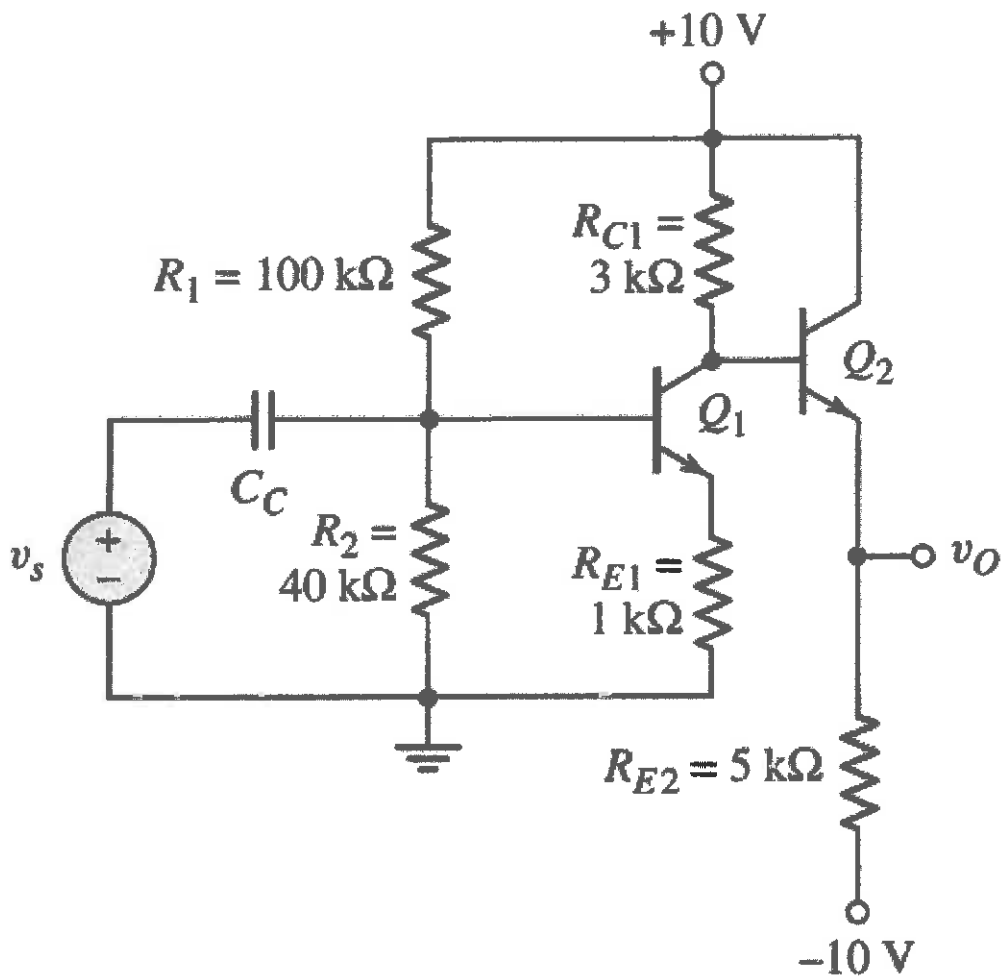


Figure 4
[Rajah 4]

Question 5*[Soalan 5]*

- (a) Power amplifiers are generally classified into Class A, Class B, Class AB and Class C.

[Penguat-penguat kuasa secara umum dikelaskan kepada Kelas A, Kelas B, Kelas AB dan Kelas C.]

- (i) Sketch and label Class B amplifier with the aid of diagram.

[Lakar dan label Kelas B penguat dengan bantuan gambarajah.]

(2 Marks/ Markah)

- (ii) Explain the operation of Class B amplifier by using a block diagram and a push-pull circuit.

[Terangkan operasi penguat Kelas B dengan menggunakan gambarajah blok dan litar tolak-tarik.]

(8 Marks/ Markah)

- (b) **Figure 5** shows Class AB amplifier operation using enhancement-mode MOSFET and the transistors are matched. Given $V_{DD} = 10\text{ V}$, $R_L = 20\ \Omega$, $K = 0.20\text{ A/V}^2$, $|V_T| = 1\text{ V}$ and I_{DQ} is increased 20 percent of the load current when $V_o = 5\text{ V}$.

[Rajah 5 menunjukkan peringkat penguat kuasa menggunakan MOSFET mod peneguhan dan transistor-transistor adalah sepadan. Diberi $V_{DD} = 10\text{ V}$, $R_L = 20\ \Omega$, $K = 0.20\text{ A/V}^2$, $|V_T| = 1\text{ V}$. I_{DQ} adalah bertambah sebanyak 20 peratus daripada arus beban apabila $V_o = 5\text{ V}$.]

- (i) State the class of power amplifier configuration in **Figure 5**.

[Nyatakan kelas bagi konfigurasi penguat dalam Rajah 5.]

(2 Marks/ Markah)

- (ii) Determine the quiescent drain current, I_{DQ} .

[Tentukan arus longkang sepi, I_{DQ} .]

(2 Marks/ Markah)

- (iii) Calculate the gate-to-source voltage, V_{GSn} of M_n transistor.

[Kirakan voltan pintu sumber, V_{GSn} bagi transistor M_n .]

(2 Marks/ Markah)

- (iv) Calculate the source-to-gate voltage, V_{SGp} of M_p transistor.

[Kirakan voltan sumber pintu, V_{SGp} bagi transistor M_p .]

(2 Marks/ Markah)

- (v) Determine the input voltage, v_i .

[Tentukan voltan masukan, v_i .]

(2 Marks/ Markah)

....11/-

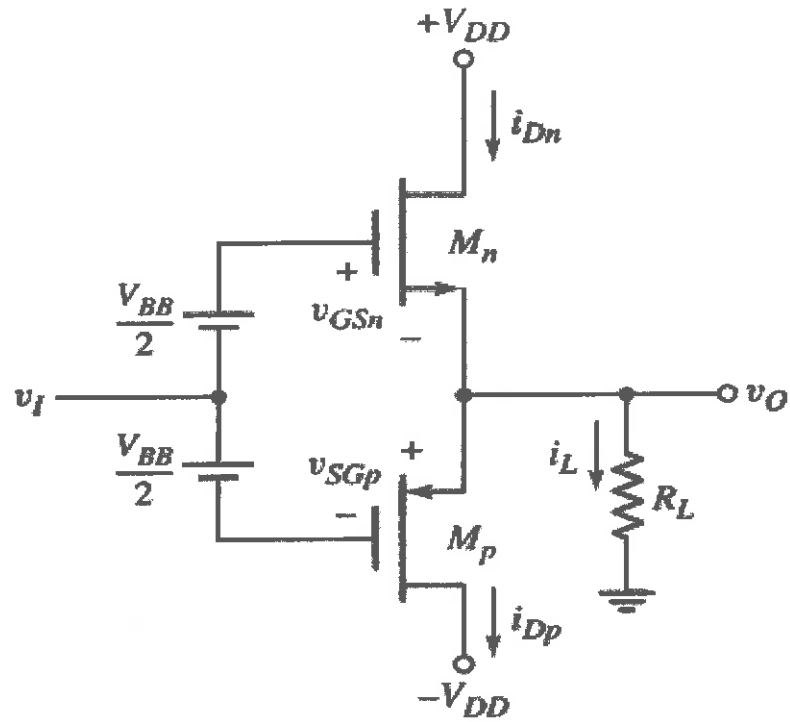


Figure 5
[Rajah5]

Question 6*[Soalan 6]*

- (a) Define the following terms:
[Takrifkan terma-terma berikut:]
- (i) Depletion mode of MOSFET.
[Ragam susutan bagi MOSFET.] (2 Marks/ Markah)
- (ii) Enhancement mode of MOSFET.
[Ragam peningkatan bagi MOSFET.] (2 Marks/ Markah)
- (b) Sketch and label the transfer characteristic curve (depletion and enhancement) for MOSFET.
[Lakar dan labelkan lengkungan sifat pindahan (pengurangan dan penambahan) bagi MOSFET.] (4 Marks/ Markah)
- (c) **Figure 6(a)** shows the NMOS common-source circuit and **Figure 6(b)** referring to the DC equivalent circuit. Given $R_1 = 30 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_D = 20 \text{ k}\Omega$, $V_{DD} = 5\text{V}$, $V_{TN} = 1\text{V}$ and $K_n = 0.1 \text{ mA/V}^2$.
[Rajah 6(a) menunjukkan litar punca-sepunya NMOS dan Rajah 6(b) merujuk kepada litar setara AT. Diberi $R_1 = 30 \text{ k}\Omega$, $R_2 = 20 \text{ k}\Omega$, $R_D = 20 \text{ k}\Omega$, $V_{DD} = 5\text{V}$, $V_{TN} = 1\text{V}$, $K_n = 0.1 \text{ mA/V}^2$ dan $\lambda = 0$.]
- (i) Determine the drain current, I_D .
[Tentukan arus longkang, I_D .] (2 Marks/ Markah)
- (ii) Calculate the drain-to-source voltage, V_{DS} .
[Kirakan voltan longkang-sumber, V_{DS} .] (3 Marks/ Markah)
- (iii) Evaluate the power dissipated in the transistor.
[Nilaiakan kuasa terlesap pada transistor.] (3 Marks/ Markah)
- (iv) Sketch and label the dc load line
[Lakar dan labelkan garis beban AT.] (4 Marks/ Markah)

....13/-

SULIT

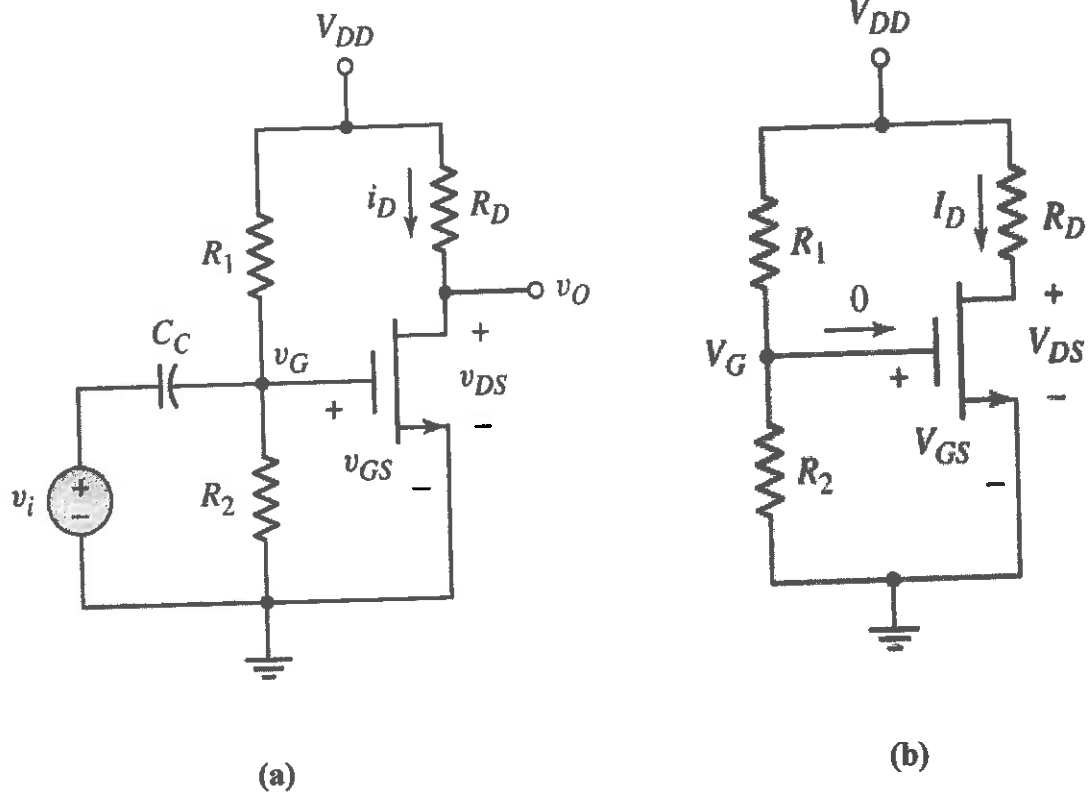


Figure 6
[Rajah 6]

-ooOoo-

Appendix

[Lampiran]

1. $g_m = \frac{I_{CQ}}{V_T}$
2. $g_m = 2K_n(V_{GS} - V_{TN})$
3. $g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right)$
4. $A_v = -g_m R_C \left(\frac{r_\pi}{r_\pi + R_D}\right)$
5. $A_v = -g_m \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{(R_1 \parallel R_2 \parallel r_\pi) + R_S}\right) (R_C \parallel r_o)$
6. $A_v = -\frac{\beta R_C}{r_\pi + (1 + \beta)R_E} \left(\frac{R_i}{R_i + R_S}\right)$
7. $A_v = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)} \left(\frac{R_i}{R_i + R_S}\right)$
8. $A_v = g_m \left(\frac{R_C \parallel R_L}{R_S}\right) \left(\frac{r_\pi}{1 + \beta} \parallel R_E \parallel R_S\right)$
9. $A_v = -g_m (r_o \parallel R_D)$
10. $A_v = \frac{-g_m (r_o \parallel R_D \parallel R_L)}{1 + g_m R_S}$
11. $A_v = -g_m (r_o \parallel R_D \parallel R_L) \left(\frac{R_i}{R_i + R_{Si}}\right)$
12. $A_v = \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)} \left(\frac{R_i}{R_i + R_{Si}}\right)$
13. $A_v = \frac{g_m (r_o \parallel R_D \parallel R_L)}{1 + g_m R_{Si}}$
14. $A_v = -g_m (r_o \parallel R_D \parallel R_L)$
15. $A_v = \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)}$
16. $I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$
17. $I_D = K_n (V_{GS} - V_{TN})^2$
18. $V_{DS(sat)} = V_{GS} - V_{TN}$