

**SULIT**

---

**UNIVERSITI MALAYSIA PERLIS**

Peperiksaan Akhir Semester Pertama  
Sidang Akademik 2018/2019

Oktober 2018

**DMT 231 – Analogue Electronics**  
**[Elektronik Analog]**

Masa: 3 jam

---

Please make sure that this question paper has **FOURTEEN (14)** printed pages including this front page before you start the examination.

*[Sila pastikan kertas soalan ini mengandungi **EMPAT BELAS (14)** muka surat yang bercetak termasuk muka hadapan sebelum anda memulakan peperiksaan ini.]*

This question paper has **TWO (2)** Parts.

*[Kertas soalan ini mempunyai **DUA (2)** bahagian.]*

**Part A** : This part has **FOUR (4)** questions. Answer all questions (80 marks).  
*[Bahagian A : Bahagian ini mengandungi **EMPAT (4)** soalan. Jawab semua soalan (80 markah).]*

**Part B** : This part has **TWO (2)** questions. Answer any **ONE (1)** question (20 marks).  
*[Bahagian B : Bahagian ini mengandungi **DUA (2)** soalan. Jawab mana-mana **SATU (1)** soalan (20 markah).]*

Each question contributes **TWENTY (20)** marks.

*[Setiap soalan menyumbang **DUA PULUH (20)** markah.]*


List of equation is given in Appendix.

*[Senarai persamaan-persamaan diberikan pada Lampiran.]*

**SULIT**

**Part A***[Bahagian A]***Answer all questions.***[Jawab semua soalan.]***Question 1***[Soalan 1]*

- (a) Sketch and label the symbols of Bipolar Junction Transistor (BJT). Write the equation for each current flow.  
*[Lakar dan labelkan simbol-simbol bagi Transistor Simpangan Dwipolar (BJT). Tuliskan persamaan bagi setiap aliran arus.]*  
(4 Marks/ Markah)
- (b) State **THREE (3)** basic types of BJT amplifiers that you know.  
*[Nyatakan **TIGA (3)** jenis penguat BJT asas yang kamu tahu.]*  
(3 Marks/ Markah)
- (c) Sketch and label the I-V characteristic curve for BJT.  
*[Lakar dan labelkan lengkungan sifat I-V bagi BJT.]*  
(4 Marks/ Markah)
- (d) Refer to **Figure 1**, assume  $\beta = 50$  and  $I_E = 2.2 \text{ mA}$ . Determine;  
*[Rujuk Rajah 1, andaikan  $\beta = 50$  dan  $I_E = 2.2 \text{ mA}$ . Tentukan;]*
- (i) quiescent base current,  $I_{BQ}$ .  
*[arus tapak sepi,  $I_{BQ}$ .]*  
(2 Marks/ Markah)
  - (ii) quiescent collector current,  $I_{CQ}$ .  
*[arus pemungut sepi,  $I_{CQ}$ .]*  
(2 Marks/ Markah)
  - (iii) base voltage,  $V_{BB}$ .  
*[voltan asas,  $V_{BB}$ .]*  
(3 Marks/ Markah)
  - (iv) quiescent collector-emitter voltage,  $V_{CEQ}$ .  
*[voltan pemungut-pemancar sepi,  $V_{CEQ}$ .]*  
(2 Marks/ Markah)

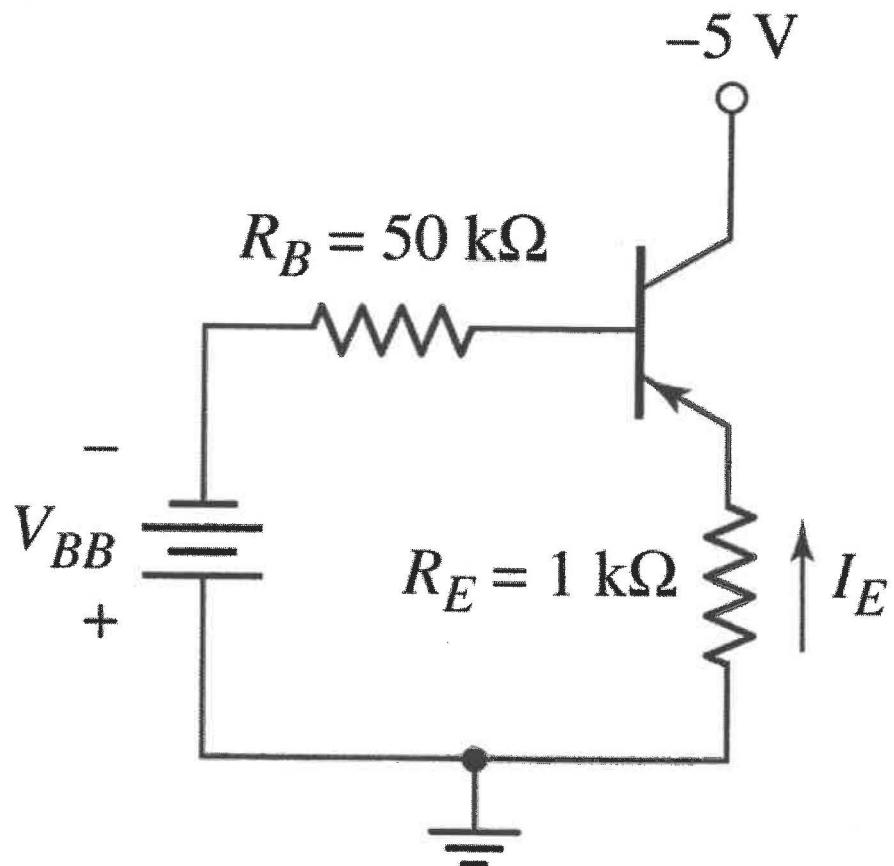


**Figure 1**  
*[Rajah 1]*

**Question 2**

[Soalan 2]

- (a) State **THREE (3)** types of Field Effect Transistor (FET).  
*[Nyatakan TIGA (3) jenis-jenis Transistor Kesan Medan (FET).]*  
(3 Marks/ Markah)
- (b) Sketch the structure and symbol for the both channels Junction Field Effect Transistor (JFET).  
*[Lakarkan struktur dan simbol bagi kedua-dua saluran Simpang Transistor Kesan Medan (JFET).]*  
(4 Marks/ Markah)
- (c) **Figure 2** show JFET amplifier for common source circuit.  
*[Rajah 2 menunjukkan penguat JFET untuk litar sumber biasa.]*
- (i) Sketch the small-signal equivalent circuit for the circuit.  
*[Lakarkan litar setara isyarat-kecil untuk litar tersebut.]*  
(5 Marks/ Markah)
- (ii) Based on 2(c)(i), derive the equation for  $V_i$  and  $V_o$ .  
*[Berdasarkan 2(c)(i), dapatkan persamaan untuk  $V_i$  dan  $V_o$ .]*  
(6 Marks/ Markah)
- (iii) Derive the equation for small-signal voltage gain,  $A_v = v_o / v_i$ .  
*[Dapatkan persamaan untuk voltan isyarat-kecil,  $A_v = v_o / v_i$ .]*  
(2 Marks/ Markah)

...5/-

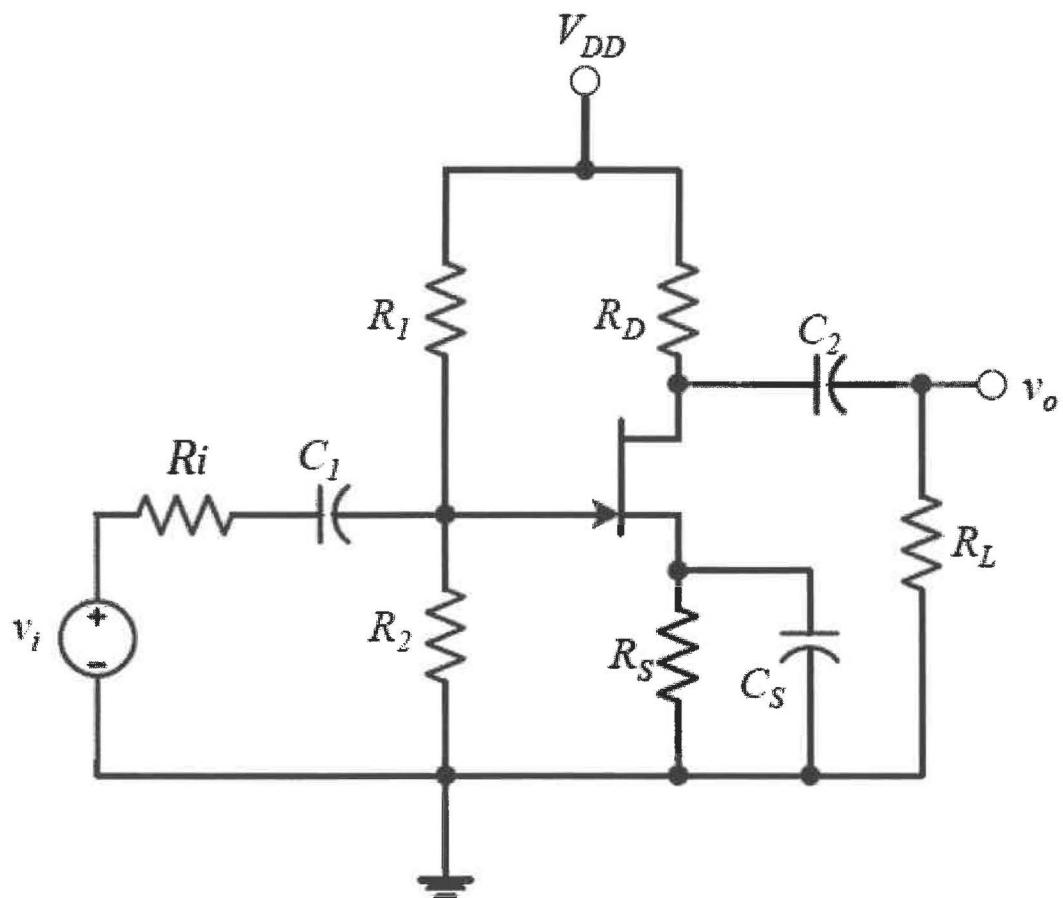

**Figure 2**  
[Rajah 2]

...6/-

SULIT

**Question 3**  
**[Soalan 3]**

- (a) **Figure 3** show a cascaded configuration as part of a multistage amplifier. The circuit elements transistor  $Q_1$  and  $Q_2$  are  $\beta_1 = \beta_2 = 100$ ,  $V_{BE(ON)} = 0.7$  V and  $V_A = \infty$ . Calculate;  
*[Rajah 3 menunjukkan konfigurasi terlatar sebagai sebahagian daripada penguat berbilang tahap. Elemen-elemen transistor  $Q_1$  dan  $Q_2$  adalah  $\beta_1 = \beta_2 = 100$ ,  $V_{BE(ON)} = 0.7$  V dan  $V_A = \infty$ . Kirakan;]*
- (i) Thevenin resistor and voltage,  $R_{TH}$  and  $V_{TH}$  for transistor  $Q_1$ .  
*[voltan dan rintangan Thevenin,  $R_{TH}$  dan  $V_{TH}$  untuk transistor  $Q_1$ .]*  
(4 Marks/ Markah)
  - (ii) the quiescent current for  $Q_1$ ,  $I_{BQ1}$  and  $I_{CQ1}$ .  
*[arus sepi bagi transistor  $Q_1$ ,  $I_{BQ1}$  dan  $I_{CQ1}$ .]*  
(2 Marks/ Markah)
  - (iii) the quiescent current for  $Q_2$ ,  $I_{BQ2}$  and  $I_{CQ2}$ .  
*[arus sepi bagi transistor  $Q_2$ ,  $I_{BQ2}$  dan  $I_{CQ2}$ .]*  
(2 Marks/ Markah)
  - (iv) diffusion resistance,  $r_{\pi 1}$  and  $r_{\pi 2}$ .  
*[rintangan resapan,  $r_{\pi 1}$  dan  $r_{\pi 2}$ .]*  
(2 Marks/ Markah)
  - (v) transconductance,  $g_{m1}$  and  $g_{m2}$   
*[trankonduktan,  $g_{m1}$  dan  $g_{m2}$ .]*  
(2 Marks/ Markah)
- (b) Sketch and label the AC equivalent circuit for multistage amplifier circuit shown in **Figure 3**.  
*[Lakar dan labelkan litar setara AU untuk litar penguat berbilang tahap yang ditunjukkan dalam Rajah 3.]*  
(4 Marks/ Markah)
- (c) Determine the small-signal voltage gain,  $A_v$ .  
*[Tentukan gandaan voltan isyarat-kecil,  $A_v$ .]*  
(4 Marks/ Markah)

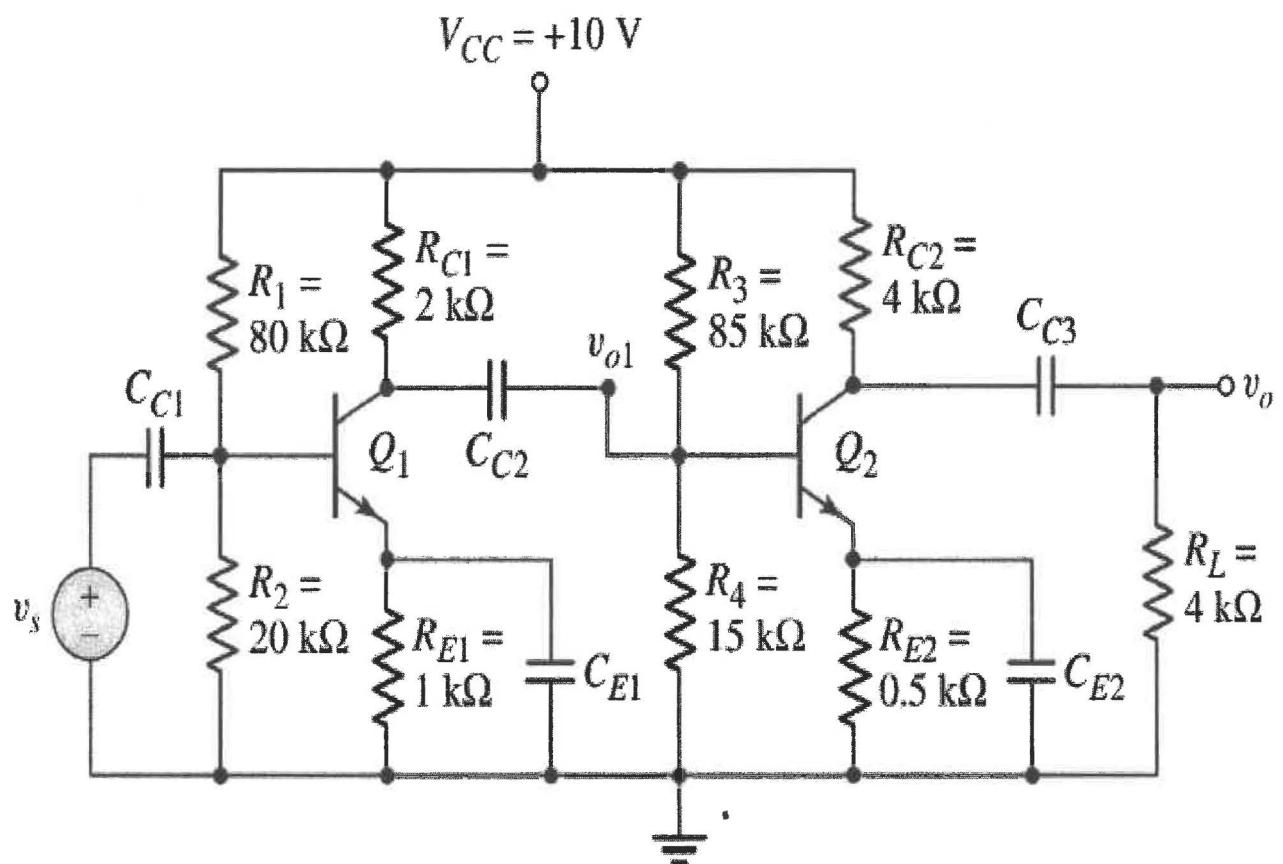


Figure 3  
[Rajah 3]

...8/-

**Question 4****[Soalan 4]**

- (a) Power amplifiers are generally classified according to the percent of time the output transistors are conducting.  
*[Penguat kuasa-penguat kuasa dikelaskan secara umum mengikut peratus masa masukan pengaliran transistor.]*
- (i) List **FOUR (4)** types classification of power amplifiers.  
*[Senaraikan EMPAT (4) kelas penguat-penguat kuasa.]*  
**(4 Marks/ Markah)**
- (ii) From **Question 4a(i)** sketch and label all class of power amplifiers.  
*[Daripada Soalan 4a(i) lukis dan labelkan semua kelas penguat-penguat kuasa.]*  
**(4 Marks/ Markah)**
- (b) **Figure 4(a)** show an operation of Class B power amplifier consists of complementary pair electronic devices. Find the condition of devices A, B and  $V_o$  when;  
*[Rajah 4(a) menunjukkan operasi Kelas B penguat kuasa terdiri daripada peranti elektronik pasangan pelengkap. Cari keadaan peranti A, B dan  $V_o$  apabila;]*
- (i)  $V_i = 0.$   
*[ $V_i = 0.$ ]*  
**(2 Marks/ Markah)**
- (ii)  $V_i > 0.$   
*[ $V_i > 0.$ ]*  
**(2 Marks/ Markah)**
- (iii)  $V_i < 0.$   
*[ $V_i < 0.$ ]*  
**(2 Marks/ Markah)**

- (c) **Figure 4(b)** referring to complementary push pull circuit for Class B operation. Assuming the transistor is in ideal condition, identify the condition of transistor  $Q_n$ ,  $Q_p$  and  $V_o$  when;

[Rajah 4(b) menunjukkan litar tarik tekan pelengkap untuk operasi Kelas B. Andaikan transistor berada pada keadaan ideal, kenalpasti keadaan transistor  $Q_n$ ,  $Q_p$  dan  $V_o$  apabila;]

(i)  $V_i = 0.$   
[ $V_i = 0.$ ]


(2 Marks/ Markah)

(ii)  $V_i > 0.$   
[ $V_i > 0.$ ]

(2 Marks/ Markah)

(iii)  $V_i < 0.$   
[ $V_i < 0.$ ]

(2 Marks/ Markah)

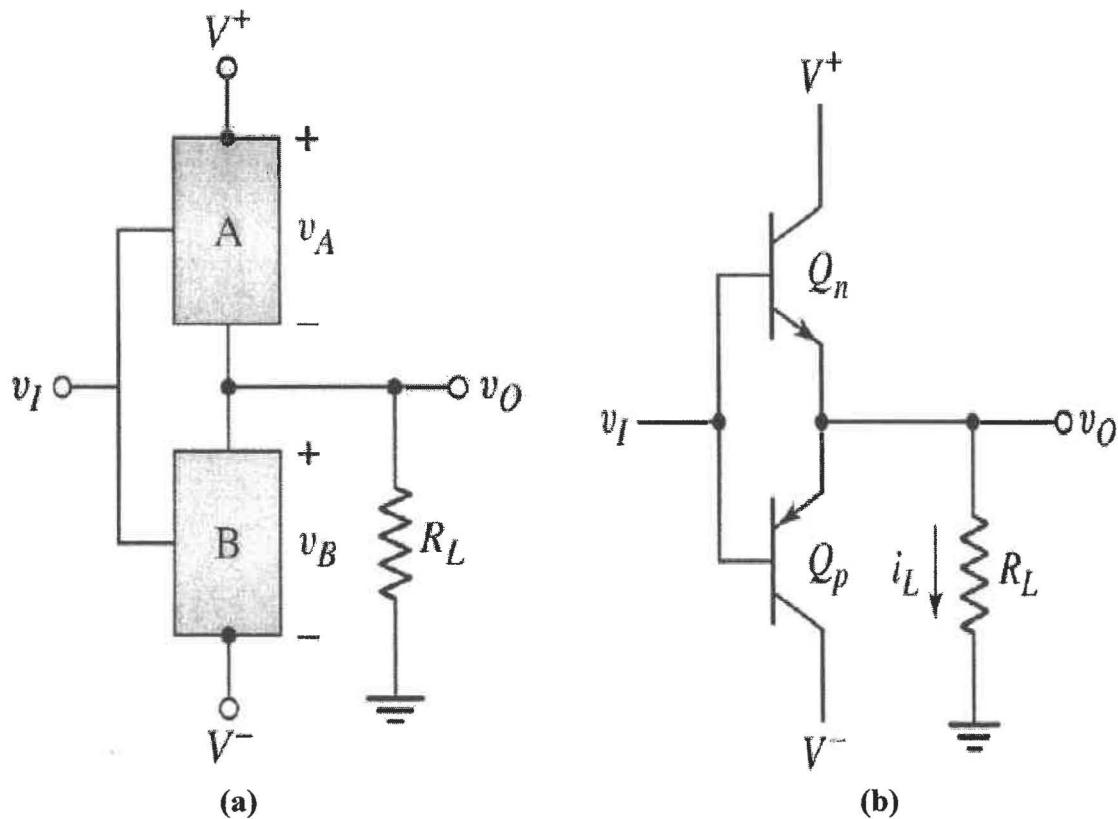

**Figure 4**  
[Rajah 4]

...10/-

**Part B***[Bahagian B]***Answer any ONE (1) question.***[Jawab mana-mana SATU (1) soalan.]***Question 5***[Soalan 5]*

- (a) **Figure 5** shows a common emitter amplifier circuit with  $\beta = 100$ ,  $V_{EB(on)} = 0.7$  V,  $V_T = 26$  mV and  $V_A = \infty$ . Evaluate;

*[Rajah 5 menunjukkan satu litar penguat pemancar sepunya dengan  $\beta = 100$ ,  $V_{EB(on)} = 0.7$  V,  $V_T = 26mV$  dan  $V_A = \infty$ . Nilaikan;]*

- (i) base current,  $I_{BQ}$ .  
*[arus tapak,  $I_{BQ}$ ]*

(3 Marks/ Markah)

- (ii) collector current,  $I_{CQ}$  and emitter-collector voltage,  $V_{ECQ}$ .  
*[arus pemungut,  $I_{CQ}$  dan voltan pemancar-pemungut,  $V_{ECQ}$ ]*

(3 Marks/ Markah)

- (iii) transconductance,  $g_m$ .  
*[trankonduktan,  $g_m$ ]*

(2 Marks/ Markah)

- (iv) diffusion resistance,  $r_\pi$  and output resistance,  $r_o$ .  
*[rintangan resapan,  $r_\pi$  dan rintangan keluaran,  $r_o$ ]*

(2 Marks/ Markah)

- (b) Sketch small signal equivalent circuit for circuit configuration shown in **Figure 5**.  
*[Lakarkan litar setara isyarat-kecil bagi konfigurasi litar yang ditunjukkan dalam Rajah 5.]*  
(6 Marks/ Markah)

- (c) Calculate small-signal voltage gain,  $A_v$ .  
*[Kira isyarat-kecil gandaan voltan,  $A_v$ ]*

(4 Marks/ Markah)

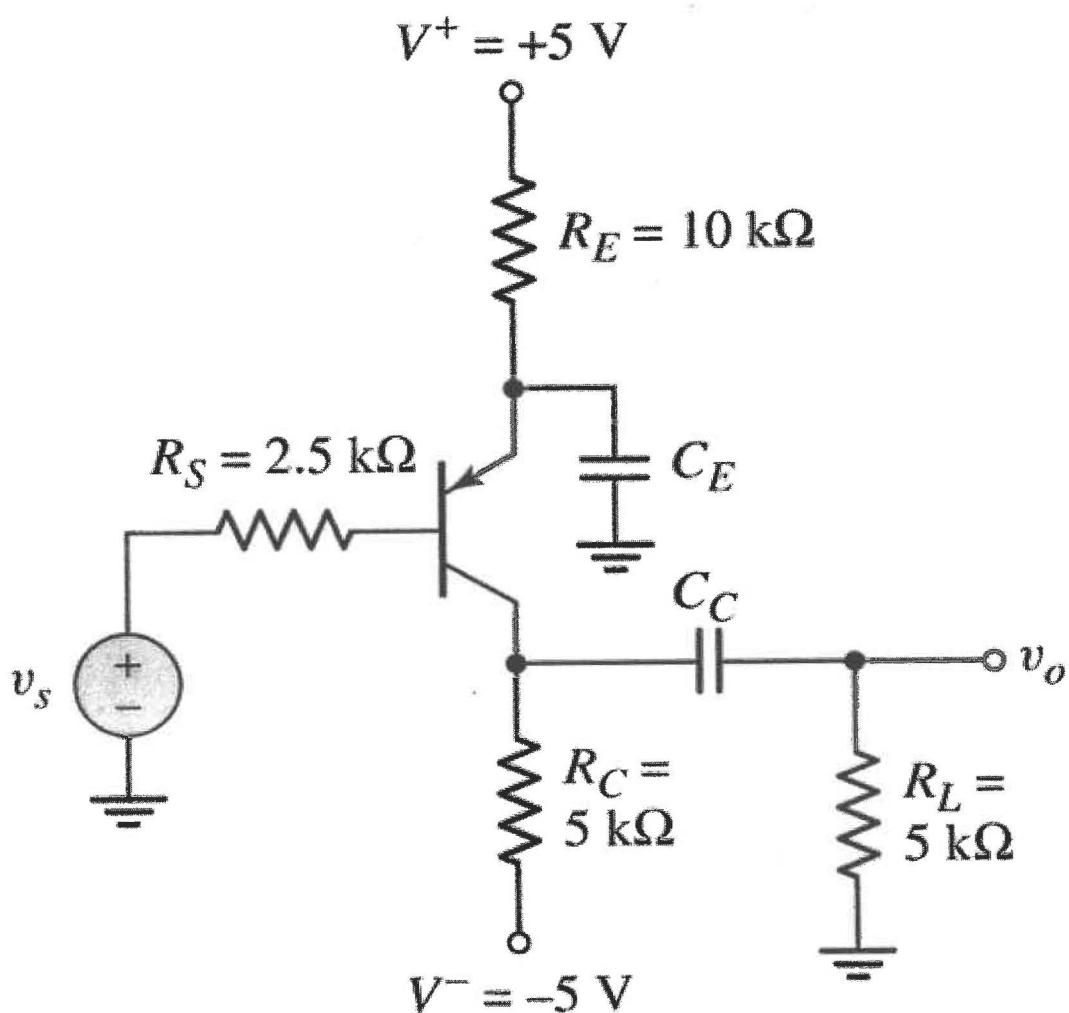


Figure 5  
[Rajah 5]

...12/-

SULIT

**Question 6**  
*[Soalan 6]*

**Figure 6** show the PMOS common-drain amplifier circuit. Given  $R_1 = 850 \text{ k}\Omega$ ,  $R_2 = 350 \text{ k}\Omega$ ,  $R_S = R_D = 4 \text{ k}\Omega$ ,  $V_{DD} = 10 \text{ V}$ ,  $\lambda = 0.05 \text{ V}^{-1}$ ,  $V_{TP} = -1.2 \text{ V}$  and  $K_p = 0.6 \text{ mA/V}^2$ .

*[Rajah 6 menunjukkan litar punca-sepunya PMOS. Diberi  $R_1 = 850 \text{ k}\Omega$ ,  $R_2 = 350 \text{ k}\Omega$ ,  $R_S = R_D = 4 \text{ k}\Omega$ ,  $V_{DD} = 10 \text{ V}$ ,  $\lambda = 0.05 \text{ V}^{-1}$ ,  $V_{TP} = -1.2 \text{ V}$  dan  $K_p = 0.6 \text{ mA/V}^2$ .]*

- (a) Derive the equation and calculate;

*[Dapatkan persamaan dan kirakan;]*

- (i) gate voltage,  $V_G$ .

*[voltan pintu,  $V_G$ .]*

(2 Marks/ Markah)

- (ii) source-to-gate voltage,  $V_{SG}$ .

*[voltan sumber-pintu,  $V_{SG}$ .]*

(3 Marks/ Markah)

- (iii) drain current,  $I_{DQ}$ .

*[arus longkang  $I_{DQ}$ .]*

(2 Marks/ Markah)

- (iv) source -to- drain voltage,  $V_{SD}$ .

*[voltan sumber-longkang,  $V_{SD}$ .]*

(3 Marks/ Markah)

- (b) Sketch small signal equivalent circuit for circuit configuration shown in **Figure 6**.

*[Lakarkan litar setara isyarat-kecil bagi konfigurasi litar yang ditunjukkan dalam Rajah 6.]*

(4 Marks/ Markah)

- (c) From question 6(b), determine;

*[Daripada soalan 6(b), tentukan;]*

- (i) transconductance,  $g_m$ .

*[trankonduktan,  $g_m$ .]*

(2 Marks/ Markah)

- (ii) output resistance,  $r_o$

*[rintangan keluaran,  $r_o$ .]*


(2 Marks/ Markah)

- (iii) small-signal voltage gain,  $A_v$ .

*[isyarat-kecil gandaan voltan,  $A_v$ .]*

(2 Marks/ Markah)

...13/-

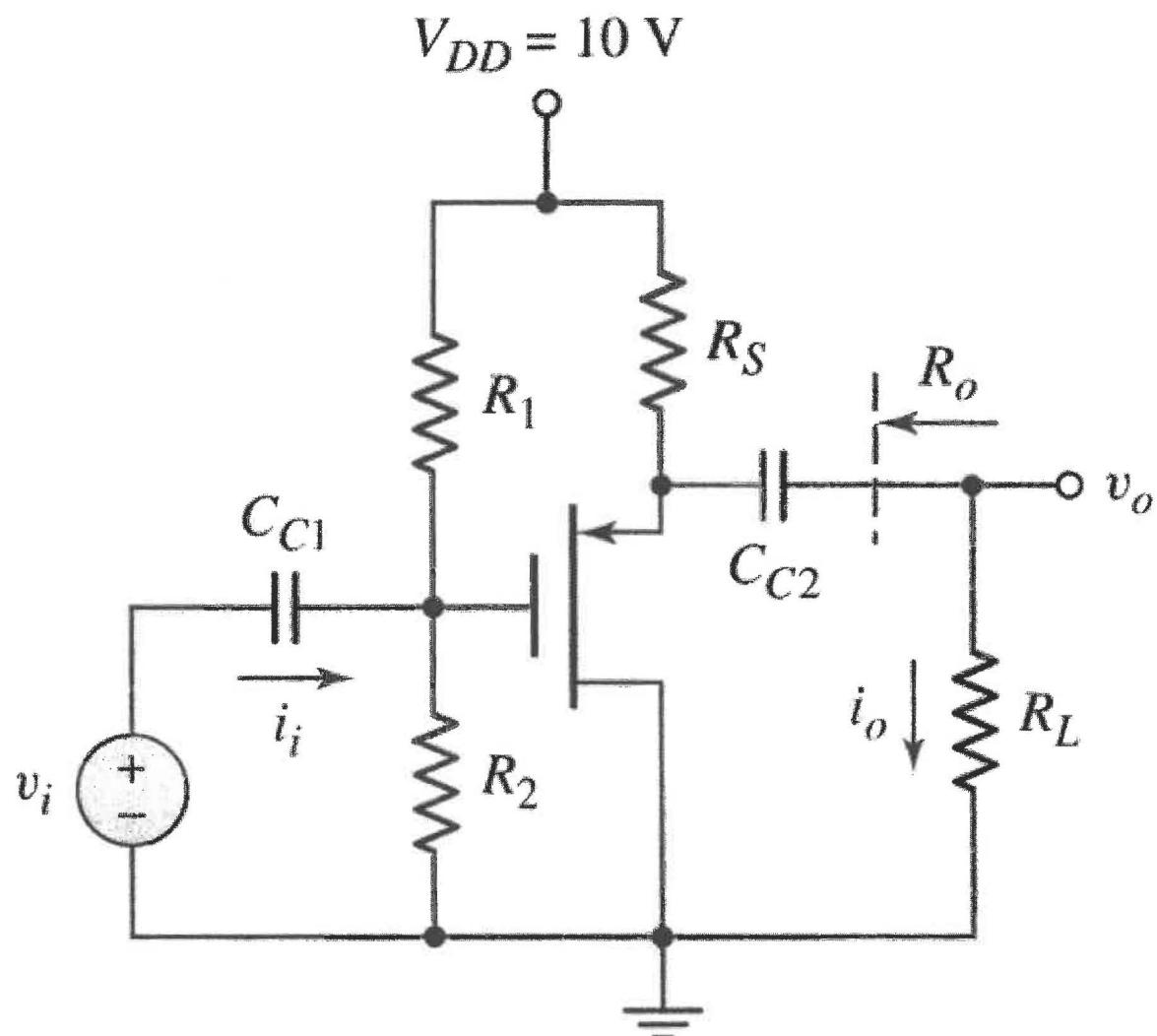

**Figure 6**  
*[Rajah 6]*

...14/-

-000Oooo-

## Appendix

*[Lampiran]*

$$1. \quad g_m = \frac{I_{CO}}{V_T}$$

$$2. \quad g_m = 2K_n(V_{GS} - V_{TN})$$

$$3. \quad g_m = \frac{2I_{DSS}}{|V_P|} \left( 1 - \frac{V_{GS}}{V_P} \right)$$

$$4. \quad A_v = -g_m R_C \left( \frac{r_\pi}{r_\pi + R_D} \right)$$

$$5. \quad A_v = -g_m \left( \frac{R_1 \parallel R_2 \parallel r_\pi}{(R_1 \parallel R_2 \parallel r_\pi) + R_S} \right) (R_C \parallel r_o)$$

$$6. \quad A_v = -\frac{\beta R_C}{r_\pi + (1 + \beta) R_E} \left( \frac{R_i}{R_i + R_S} \right)$$

$$7. \quad A_v = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)} \left( \frac{R_i}{R_i + R_S} \right)$$

$$8. \quad A_v = g_m \left( \frac{R_C \parallel R_L}{R_S} \right) \left( \frac{r_\pi}{1 + \beta} \parallel R_E \parallel R_S \right)$$

$$9. \quad A_v = -g_m (r_o \parallel R_D)$$

$$10. \quad A_v = \frac{-g_m (r_o \parallel R_D \parallel R_L)}{1 + g_m R_S}$$

$$11. \quad A_v = -g_m (r_o \parallel R_D \parallel R_L) \left( \frac{R_i}{R_i + R_{Si}} \right)$$

$$12. \quad A_v = \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)} \left( \frac{R_i}{R_i + R_{Si}} \right)$$

$$13. \quad A_v = \frac{g_m (r_o \parallel R_D \parallel R_L)}{1 + g_m R_{Si}}$$

$$14. \quad A_v = -g_m (r_o \parallel R_D \parallel R_L)$$

$$15. \quad A_v = \frac{g_m (r_o \parallel R_S \parallel R_L)}{1 + g_m (r_o \parallel R_S \parallel R_L)}$$

$$16. \quad I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$17. \quad I_D = K_N (V_{GS} - V_{TN})^2$$

$$18. \quad I_D = K_p (V_{SG} - V_{TP})^2$$

$$19. \quad V_{DS(sat)} = V_{GS} - V_{TN}$$

$$20. \quad V_{SD(sat)} = V_{SG} - V_{TP}$$